


**Introduction to  
Phase Locked Loop  
(PLL)**



# Presentation Outline

- What is Phase Locked Loop (PLL)
- Basic PLL System
- Problem of Lock Acquisition
- Phase/Frequency Detector (PFD)
- Charge Pump PLL
- Application of PLL


# What is Phase Locked Loop (PLL)

- PLL is an **Electronic Module** (Circuit) that **locks** the **phase** of the **output** to the **input**.




# Locked Vs. Unlocked Phase

- Example of locked phase

 


- Example of unlocked phase

 
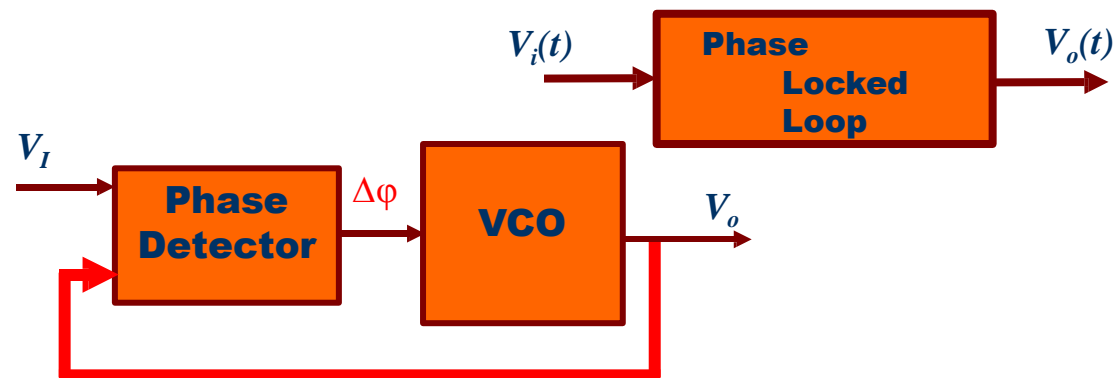
# Basic PLL System



- PLL is a **feedback** system that **detects** the **phase error  $\Delta\phi$**  and then **adjusts** the phase of the output.




- The **Phase Detector (PD)**, detects  $\Delta\phi$  between the output and the input through feedback system
- **Voltage Control Oscillator (VCO)** adjusts the phase difference

# Implementation of PD

Phase Detector is an XOR gate

  

 
$$\Delta\phi = \begin{cases} 1 & V_I \neq V_o \\ 0 & V_I = V_o \end{cases}$$


 
# What is VCO ?

- VCO is a circuit module that **oscillates** at a controlled frequency  $\omega$ .
- The **Oscillating Frequency** is controlled using Voltage  $V_{Control}$ .
  - That is why the module is called
    - **Voltage Control Oscillator**




$$\omega = \omega_0 + K_{VCO} V_{Control}$$

- $V_{control}$  must be in the **steady state** for the VCO to operate properly
 
# Simple PLL

- Structure
  - Phase Detector ( **XOR** ) that detects the phase error  $\Delta\phi$
  - Low Pass Filter ( to smooth  $\Delta\phi$  )
  - Voltage Control Oscillator (**VCO**)
- Basic Idea
  - If  $V_I$  and  $V_{out}$  are **out of phase (unlocked)**, then the **PD** module **detects** the error and the **LPF** **smooths the error signal**. The control signal **slows down** or **speeds up** the **VCO** module; hence, the **phase is corrected (locked)**






# Locked Condition

- Locked Condition

$$\frac{d}{dt}(\varphi_{in} - \varphi_{out}) = 0$$

- This implies that


$$\omega_{in} = \omega_{out}$$

 
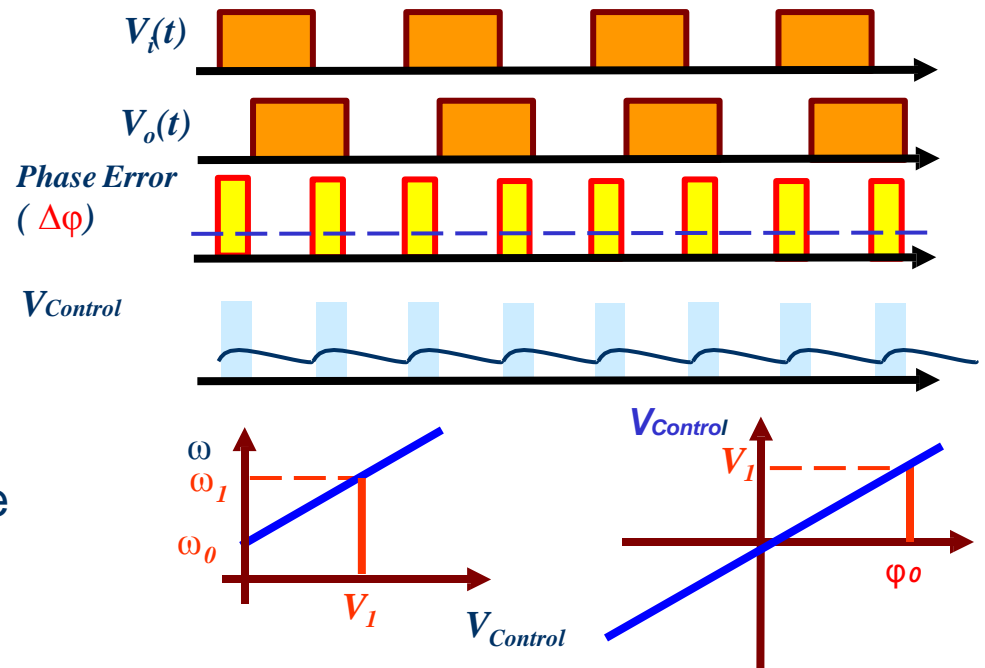
# Example: In the UNLOCKED State

$V_I$  and  $V_{out}$  has  $\Delta\phi$  at the same frequency  $\omega_1$

- The phase detector must produce  $V_I$
- Hence,  $VCO$  is dynamically changing and  $PD$  is creating  $V_{Control}$  to adjust for the phase difference.
- The PLL is in the **Locked** state



# In the UNLOCKED State

- **For Simplicity** and by using **Fourier Series**

- Let  $V_I = V_A \cos(\omega_1 t)$        $V_{out} = V_B \cos(\omega_1 t + \phi_o)$

- Due to  $\Delta\phi$ , PD creates  $V_{control}$
- VCO will change

$$\omega_{out} = \omega_1 + K_{VCO} V_{Control}$$


- The output voltage becomes

$$V_{out} = V_B \cos(\omega_1 t + \phi_o - \Delta\phi(t))$$
 
# Dynamics of Simple PLL

- PLL is a **feedback system**
  - PD is a **gain amplifier**
  - LPF be **first order filter** ( as an example)
  - VCO is a **unit step module**
- The **transfer function** of the feedback system is given as:



$$H(s) = \frac{\Phi_{out}(s)}{\Phi_{in}(s)} = \frac{\omega_{out}(s)}{\omega_{in}(s)} = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2} \quad H(s) = \frac{K_{PD}K_{VCO}\omega_{LPF}}{s^2 + \omega_{LPF}s + K_{PD}K_{VCO}\omega_{LPF}}$$


 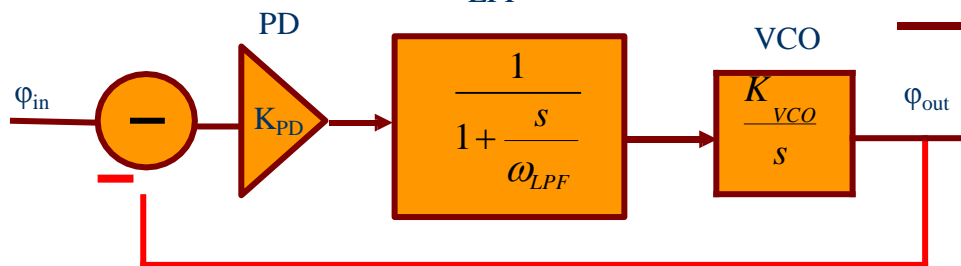
# Transient Response to PLL


- The **unit step response** to second order system
  - Overdamped
  - Critically damped
  - Underdamped
- **Problems with this PLL**
  - Settling time Vs. ripple of Vcontor
  - Stability of the system
  - Lacks performance in ICs

$$H(s) = \frac{\Phi_{out}(s)}{\Phi_{in}(s)} = \frac{\omega_{out}(s)}{\omega_{in} \text{ LPF}} = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$


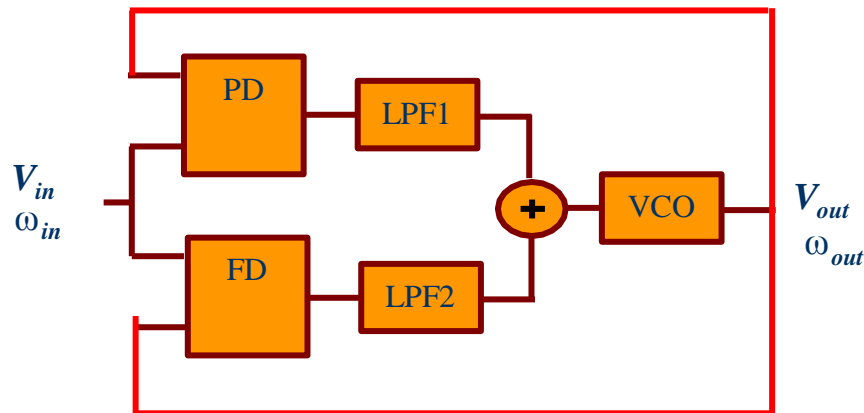
# Problem of Lock Acquisition

- When PLL is turned on, the output frequency is far from the input frequency
- It is possible that the PLL would never lock
- Modern PLL uses **FREQUENCY DEDECTOR (FD)** in addition to the **PD**.



# Phase/Frequency Detector (PFD)


- One Module that **detects both frequency and phase** differences
- This module **senses the transition** in A or B

|           | A           | B              | QA             | QB             |
|-----------|-------------|----------------|----------------|----------------|
| Initially | 0           | 0              | 0              | 0              |
| A leads B | 0 € 1<br>XX | 0 € 0<br>0 € 1 | 0 € 1<br>1 € 0 | 0 € 0<br>0 € 0 |

|           | A              | B           | QA             | QB             |
|-----------|----------------|-------------|----------------|----------------|
| Initially | 0              | 0           | 0              | 0              |
| B leads A | 0 € 0<br>0 € 1 | 0 € 1<br>XX | 0 € 0<br>0 € 0 | 0 € 1<br>0 € 0 |




 - If A leads B, **QA** changes its state and **QB** remains unchanged
- If B leads A, **QB** changes its state and **QA** remains unchanged


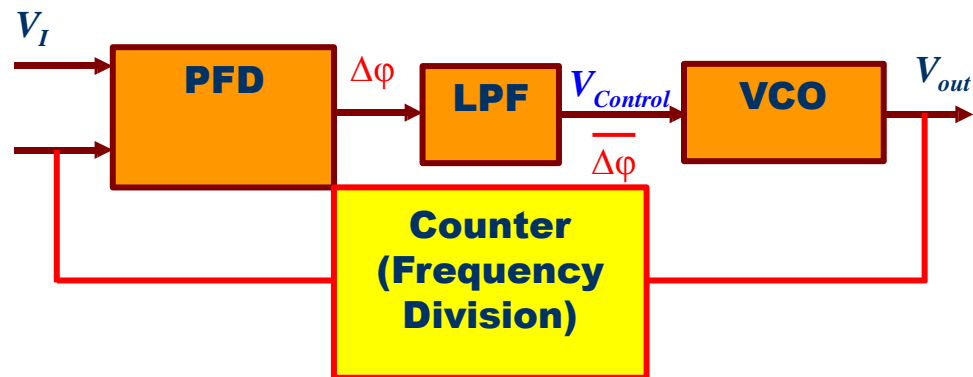
# Application of PLL

- **Frequency Multiplications**
  - The feedback loop has frequency division
  - Frequency division is implemented using a counter



## Clock Skew Reduction


Buffers are used to distribute the clock

Embed the buffer within the loop


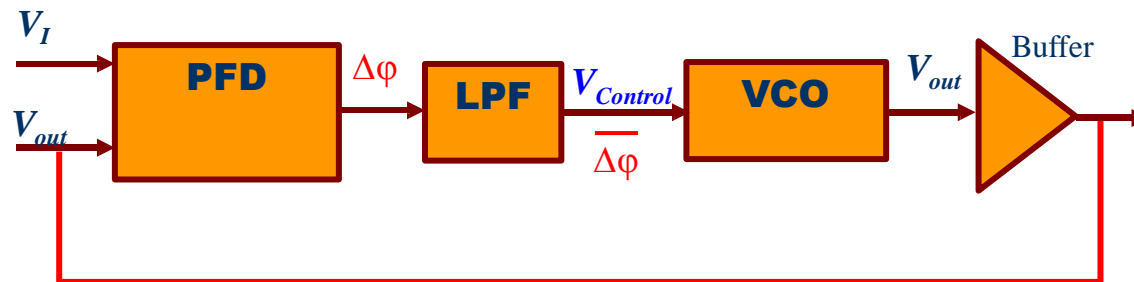
# Application of PLL

- Clock Skew Reduction
  - Buffers are used to distribute the clock
  - Embed the buffer within the loop



- Jitter Reduction