

OPERATIONAL AMPLIFIERS

- **The integrated circuit or IC is a Miniature, low cost electronic circuit consisting of active and passive components that are joined together on a single crystal chip of silicon**
- **It is a versatile device that can be used to amplify DC as well as AC input signals and was originally designed for computing such mathematical functions as Addition, Subtraction, Multiplication and Integration**

APPLICATIONS OF AN INTEGRATED CIRCUIT

➤ **Communication**

➤ **Control**

➤ **Instrumentation**

➤ **Computer**

➤ **Electronics**

ADVANTAGES

- **Small size**
- **Low cost**
- **Less weight**
- **Low supply voltages**
- **Low power consumption**
- **High reliable**
- **Matched devices**
- **Fast speed**

DISADVANTAGES

- **Most Op-amp are designed for low power operation.**
- **For high output the Op-Amp should be designed specifically.**
- **Commercial Op-Amp shuts off when the load resistance is below the specific level**

CLASIFICATION OF IC 'S

➤ **Digital IC's**

➤ **Linear IC's**

➤ **Integrated circuits**

i) Monolithic circuits

a) Bipolar

i)PN junction isolation

ii) Dielectric isolation

b) Unipolar



i) MOSFET

II) JFET

ii) Thick and Thin Film

iii) Hybrid circuits

SYMBOL OF OP-AMP

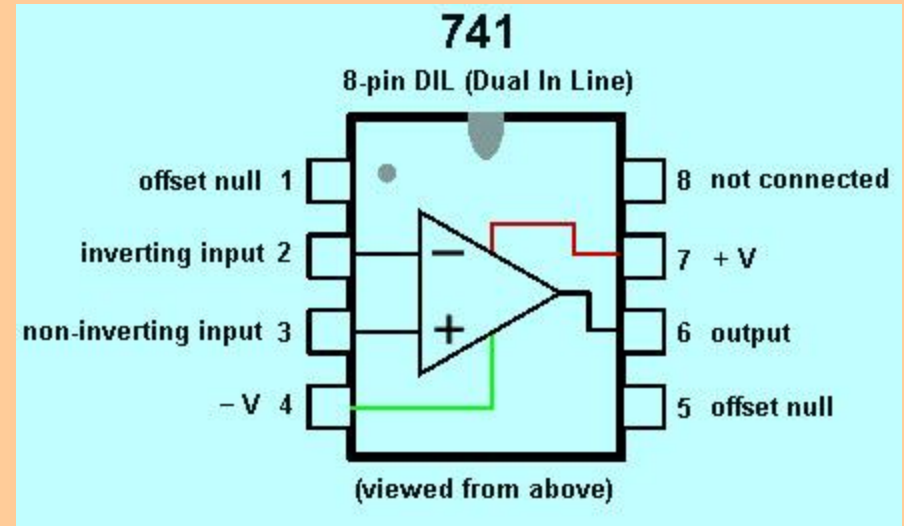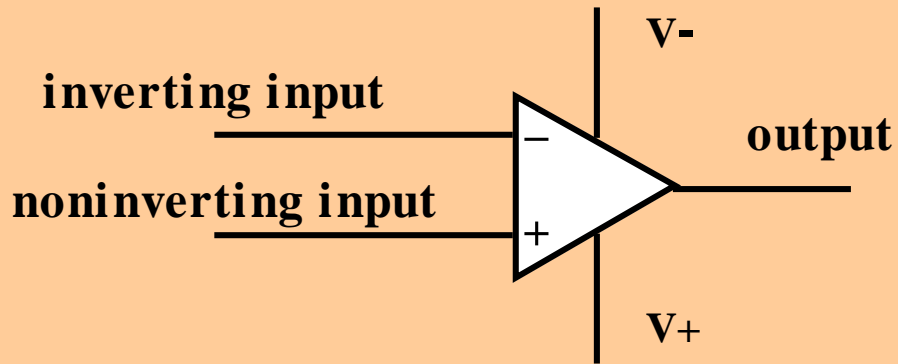

7- Terminals, 4- Input, 1-Output =IC 741

IDEAL CHARACTERISTICS OF OP-AMP

- Infinite input impedance
- Infinite open-loop gain
- Zero output impedance
- Infinite bandwidth
- Zero noise.
- It has positive and negative inputs which allow circuits that use feedback to achieve a wide range of functions.

PERFORMANCE PARAMETERS OF OP-AMP

- **Input Offset voltage**
- **Input Offset current**
- **Input bias current**
- **Differential Input resistance**
- **Open loop Voltage gain**
- **CMRR**
- **Output resistance**
- **Input voltage range**
- **Power supply rejection ratio**
- **Power consumption**
- **Slew rate**
- **Gain**
- **Output offset voltage**

INPUT OFFSET VOLTAGE

- It is defined as the **voltage** that must be applied between the two **input** terminals of an **OPAMP** to null or zero the output.
- The input offset voltage of IC741 Op-Amp is 6mv

INPUT OFFSET CURRENT

- The algebraic difference between the currents flowing into the two input terminals of the Op-Amp.
- The input offset current of IC741 Op-Amp is 200nA

INPUT BIAS CURRENT

- **The average value of the two currents flowing into the Op-Amp input terminals.**
- **The input bias current of IC741 Op-Amp is 500nA**

DIFFERENTIAL INPUT RESISTANCE

- **It is the equivalent resistance measured at either the Inverting or Non-Inverting Input terminal with the other Input terminal grounded.**
- **The Differential Input Resistance of IC741 Op-Amp is 2M Ω**

OPEN LOOP VOLTAGE GAIN

➤ It is the ratio of output voltage to the differential input voltage.

➤ It is denoted by $AOL = V_o/V_d$

➤ The Open loop Voltage gain of IC741 Op-Amp is typically 200,000

CMRR

➤ It is the ratio of differential voltage gain A_d to the Common mode voltage gain A_c .

➤ It is denoted by $CMRR = A_d/A_c$

➤ The CMRR of IC741 Op-Amp is 90db

OUTPUT RESISTANCE

- **It is the equivalent resistance measured between the output terminal of the Op-Amp and Ground.**
- **It is denoted by R_o .**
- **The Output Resistance of IC741 Op-Amp is 75Ω**

INPUT VOLTAGE RANGE

- **It is the range of a common mode input signal for which a differential amplifier remains linear.**
- **The Input Voltage Range of IC741 Op-Amp is $\pm 13V$**

POWER SUPPLY REJECTION RATIO

- **It is defined as the ratio of the change in supply voltage to the equivalent (differential) output voltage it produces.**
- **The Power Supply Rejection Ratio of IC741 Op-Amp is $30 \mu\text{V/V}$**

POWER CONSUMPTION

- **It is the amount of quiescent power to be consumed by Op-Amp with zero input voltage, for its proper functioning.**
- **The Power Consumption of IC741 Op-Amp is 85mW.**

SLEW RATE

- **It is defined as the maximum rate of change of output voltage with time.**

GAIN


- **It is the bandwidth of an Op-Amp when voltage gain is unity.**
- **The Gain of IC741 Op-Amp is 1MHz**

OUTPUT OFFSET VOLTAGE

- **It is the DC voltage present at the Output terminals when both the input terminals are grounded**


ISOLATION OR VOLTAGE FOLLOWER.

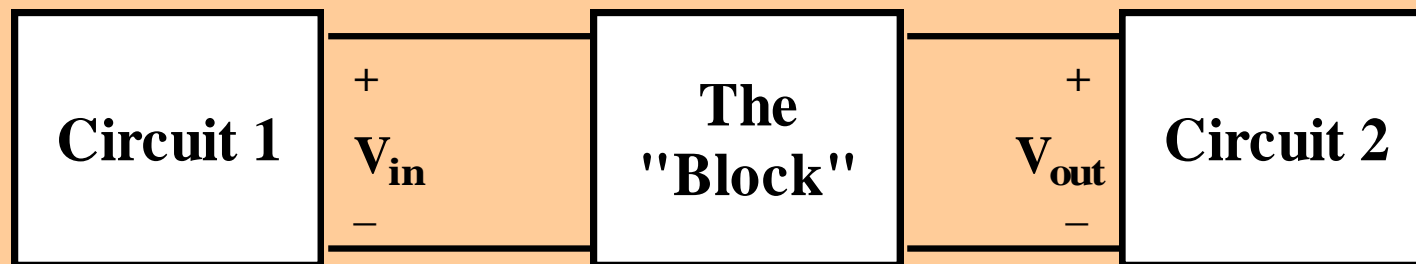➤ Applications arise in which we wish to connect one circuit to another without the first circuit loading the second. This requires that we connect to a “block” that has infinite input impedance and zero output impedance. An operational amplifier does a good job of approximating this. Consider the following:



Illustrating Isolation.


ISOLATION OR VOLTAGE FOLLOWER...

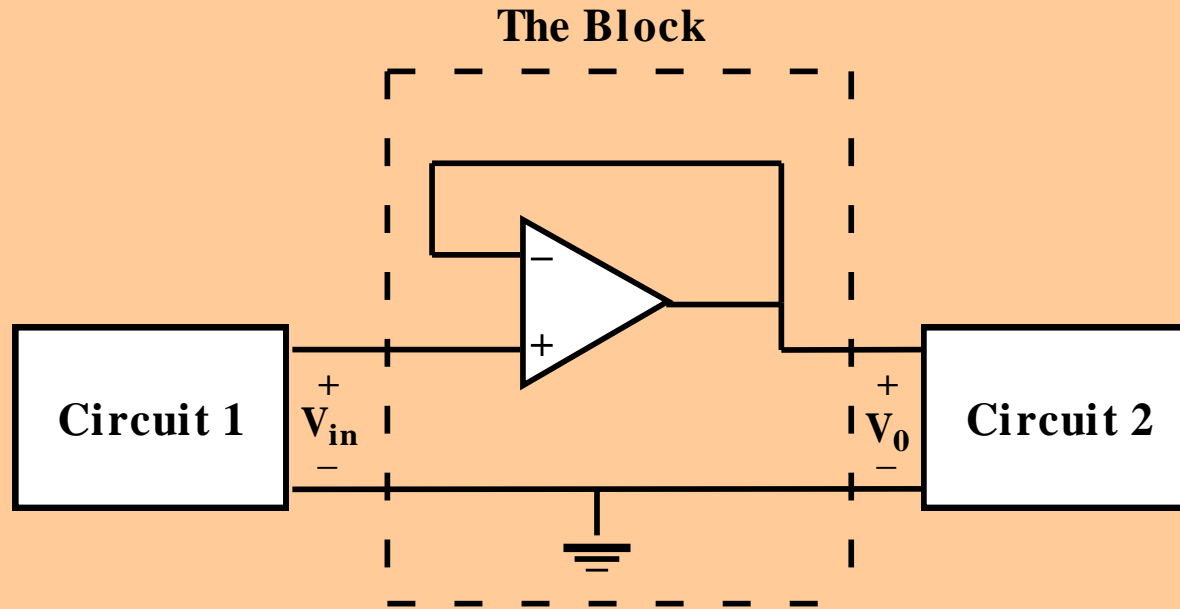

Circuit isolation with an op amp.

It is easy to see that: $V_0 = V_{in}$

NONINVERTING OP AMP

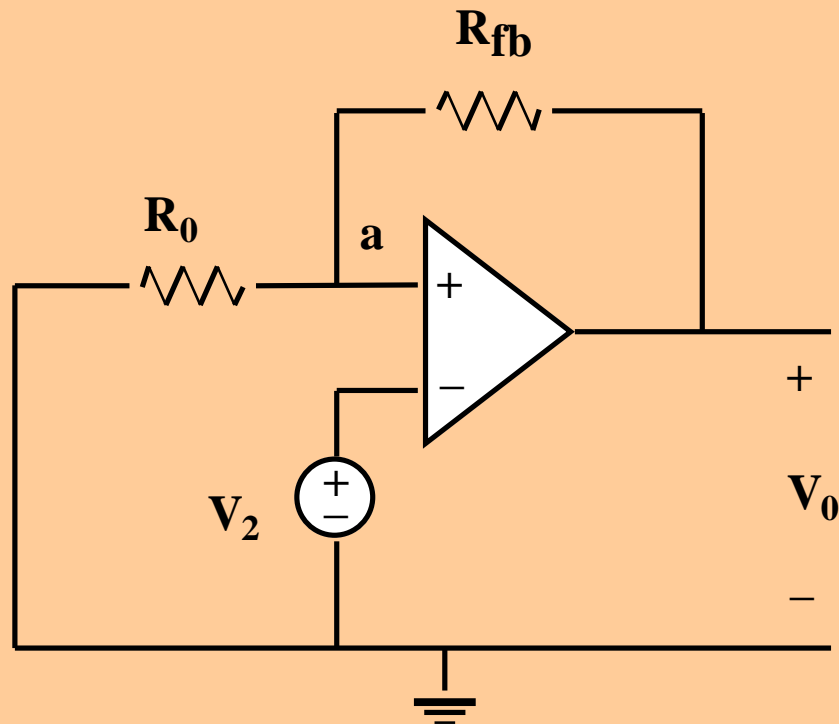

Non-inverting op amp configuration.

NON- INVERTING OP AMP...

Writing a node equation at “a” gives;

$$\frac{V_2}{R_0} + \frac{(V_2 - V_0)}{R_{fb}} = 0$$


so

$$\frac{V_0}{R_{fb}} = V_2 \left[\frac{1}{R_0} + \frac{1}{R_{fb}} \right]$$

which gives,


$$V_0 = \left(1 + \frac{R_{fb}}{R_0} \right) V_2$$

INVERTING OP AMP

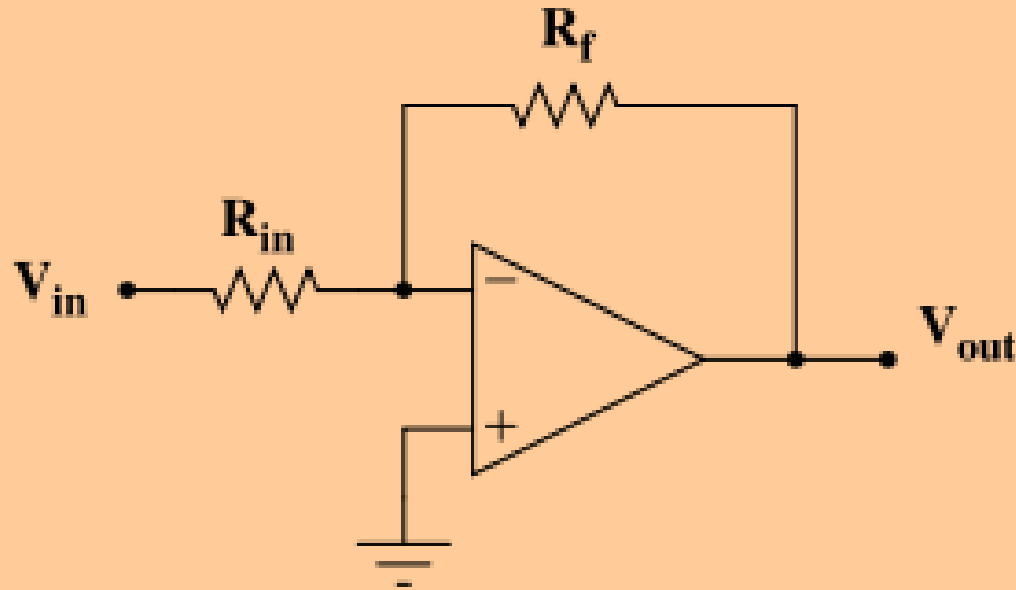

$$V_{out} = -V_{in} \left(\frac{R_f}{R_{in}} \right)$$

INTEGRATOR

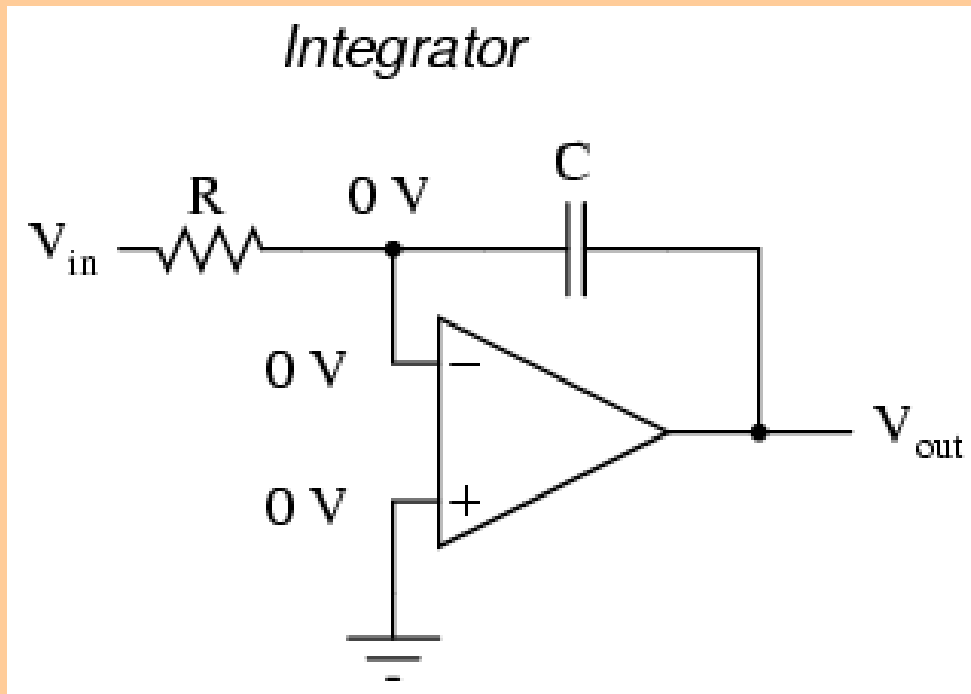

$$\frac{dv_{out}}{dt} = - \frac{V_{in}}{RC}$$


or

$$V_{out} = \int_0^t \frac{V_{in}}{RC} dt + c$$

Where,

$c =$ Output voltage at start time ($t=0$)

DIFFERENTIATOR

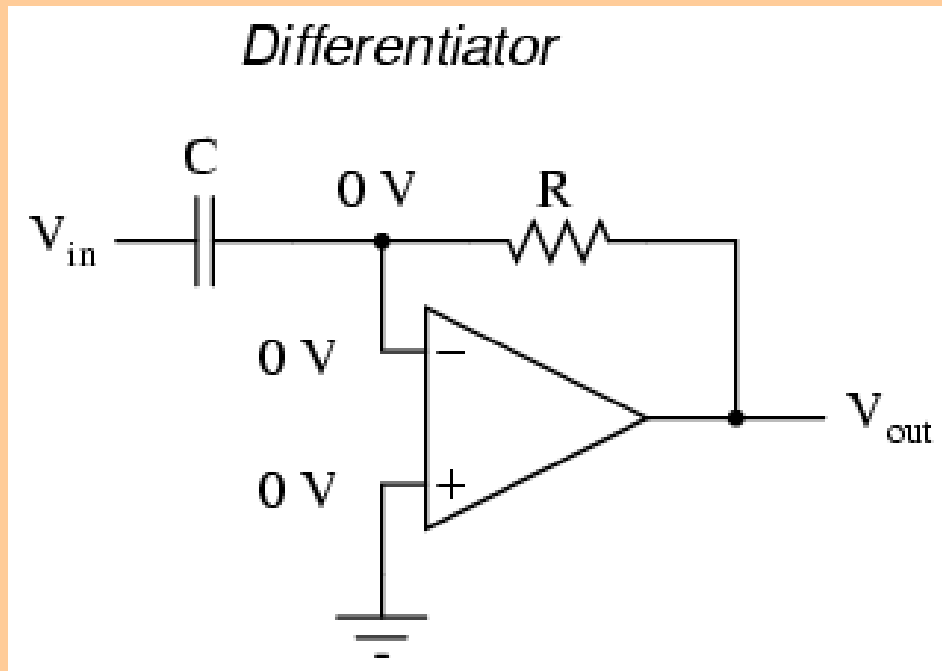

$$V_{out} = -RC \frac{dv_{in}}{dt}$$