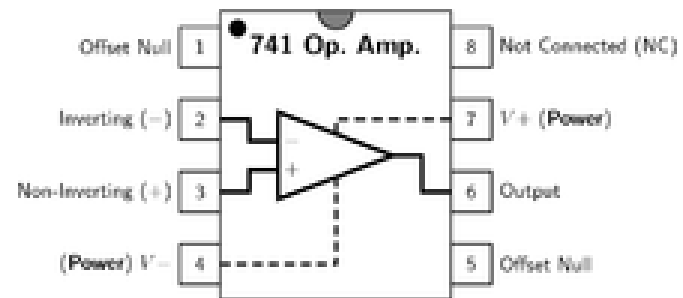


# What is an Op-Amp? – The Surface

- An Operational Amplifier (Op-Amp) is an integrated circuit that uses external voltage to amplify the input through a very high gain.
- We recognize an Op-Amp as a mass-produced component found in countless electronics.




What an Op-Amp looks like to a lay-person



What an Op-Amp looks like to an engineer

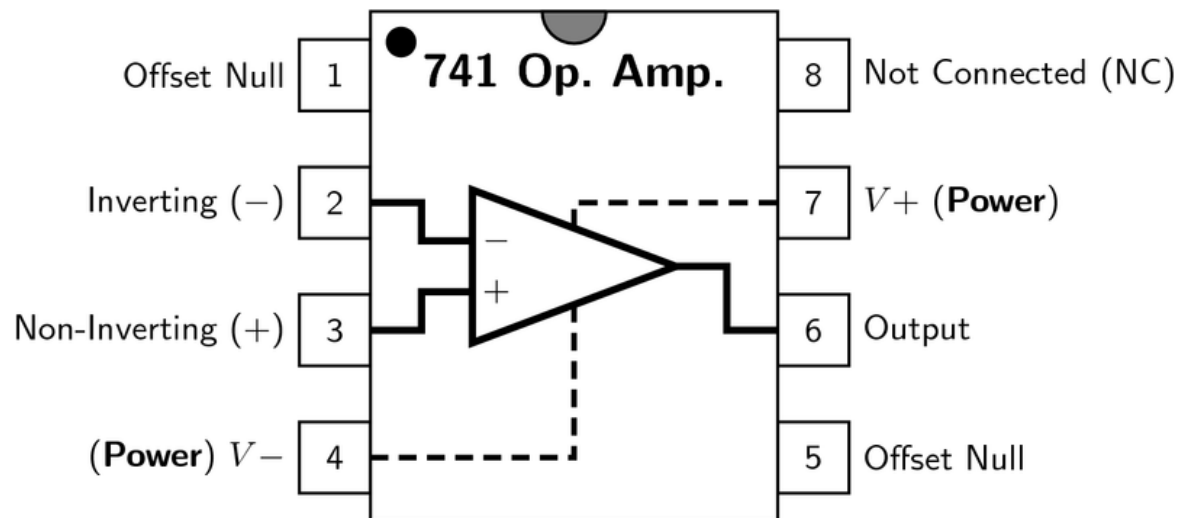
# What is an Op-Amp? – The Layout

- There are 8 pins in a common Op-Amp, like the 741 which is used in many instructional courses.



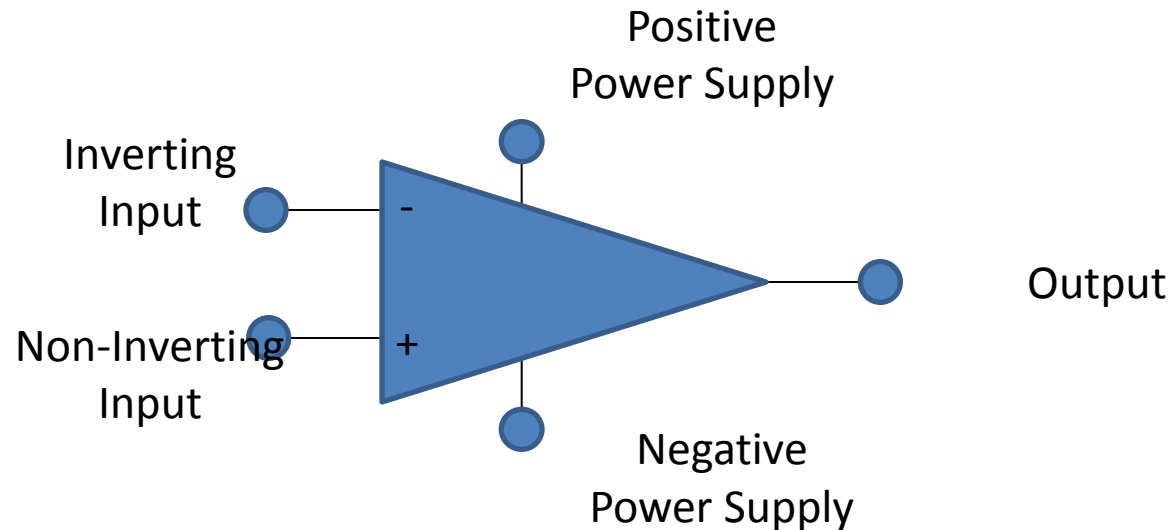
# What is an Op-Amp? – The Inside

- The actual count varies, but an Op-Amp contains several Transistors, Resistors, and a few Capacitors and Diodes.
- For simplicity, an Op-Amp is often depicted as this:


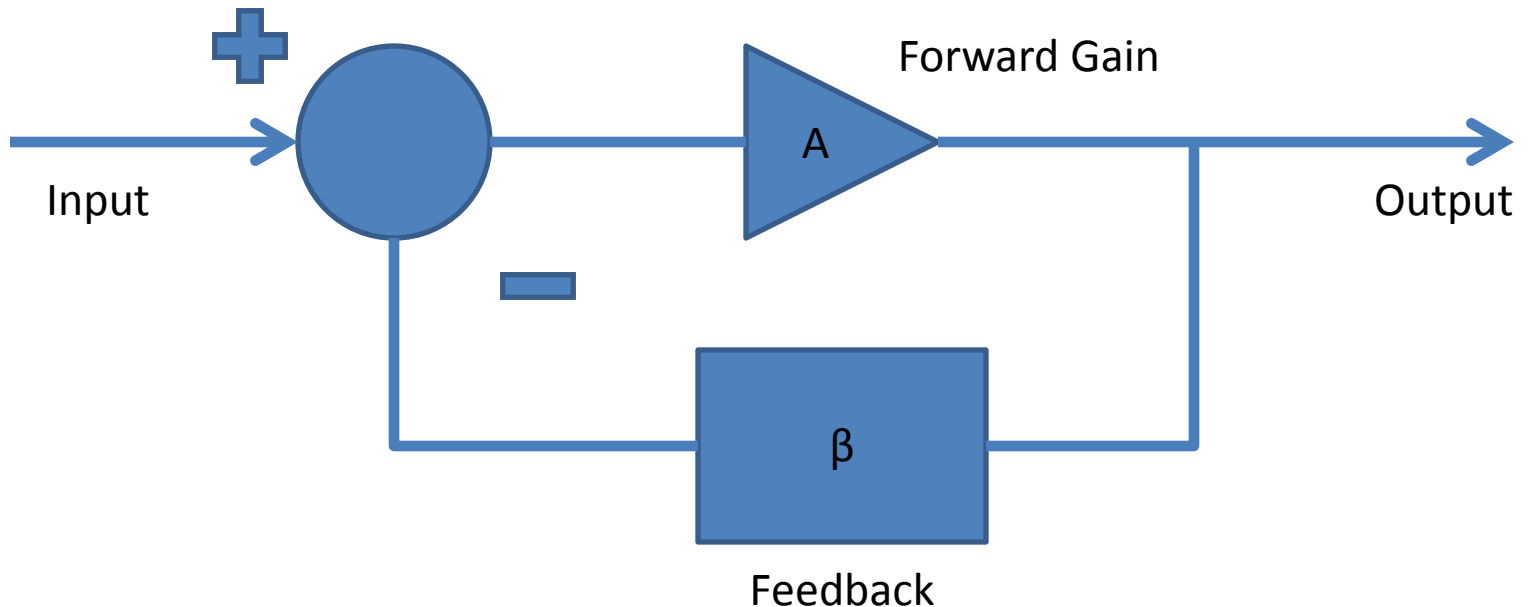
# History of the Op-Amp – The Dawn


- Before the Op-Amp: Harold S. Black develops the feedback amplifier for the Western Electric Company (1920-1930)


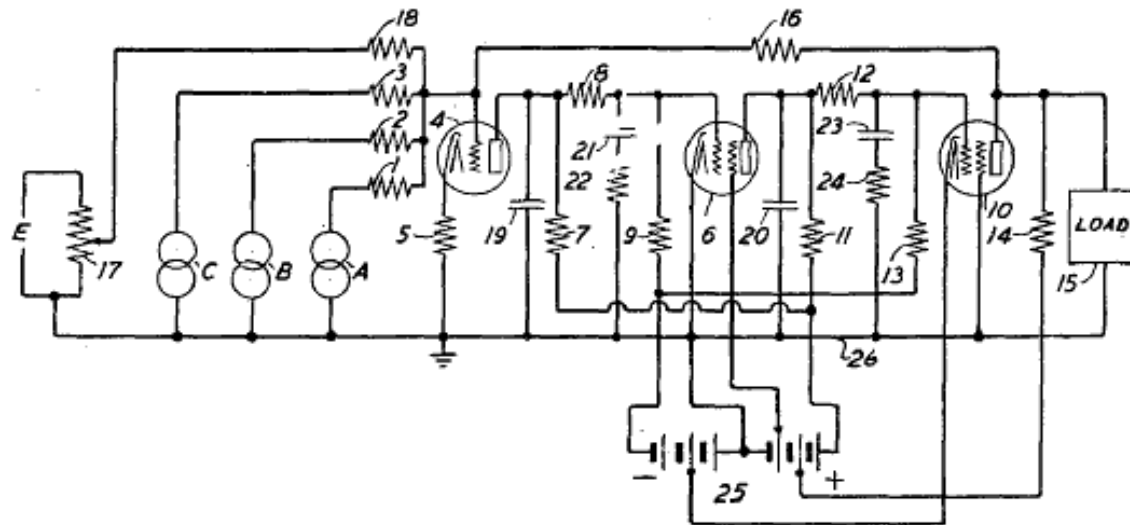
# History of the Op-Amp – The Dawn

- **The Vacuum Tube Age**

- The First Op-Amp: (1930 – 1940) Designed by Karl Swartzel for the Bell Labs M9 gun director
- Uses 3 vacuum tubes, only one input, and  $\pm 350$  V to attain a gain of 90 dB
- Loebe Julie then develops an Op-Amp with two inputs: Inverting and Non-inverting



# History of the Op-Amp – The Shift

- The end of Vacuum Tubes was built up during the 1950's-1960's to the advent of solid-state electronics

1. The Transistor
2. The Integrated Circuit
3. The Planar Process

# History of the Op-Amp – The Shift

- 1960s: beginning of the Solid State Op-Amp
- Example: GAP/R P45 (1961 – 1971)
  - Runs on  $\pm 15$  V, but costs \$118 for 1 – 4
- The GAP/R PP65 (1962) makes the Op-Amp into a circuit component as a potted module



# History of the Op-Amp – The Evolution

- The solid-state decade saw a proliferation of Op-Amps
  - Model 121, High Speed FET family, etc.
- Robert J. Widlar develops the  $\mu$ A702 Monolithic IC Op-Amp (1963) and shortly after the  $\mu$ A709
- Fairchild Semiconductor vs. National Semiconductor
  - National: The LM101 (1967) and then the LM101A (1968) (both by Widlar)
  - Fairchild: The “famous”  $\mu$ A741 (by Dave Fullager 1968) and then the  $\mu$ A748 (1969)



# Mathematics of the Op-Amp

- The gain of the Op-Amp itself is calculated as:


$$G = V_{\text{out}} / (V_{+} - V_{-})$$

- The maximum output is the power supply voltage
- When used in a circuit, the gain of the circuit (as opposed to the op-amp component) is:


$$A_v = V_{\text{out}} / V_{\text{in}}$$
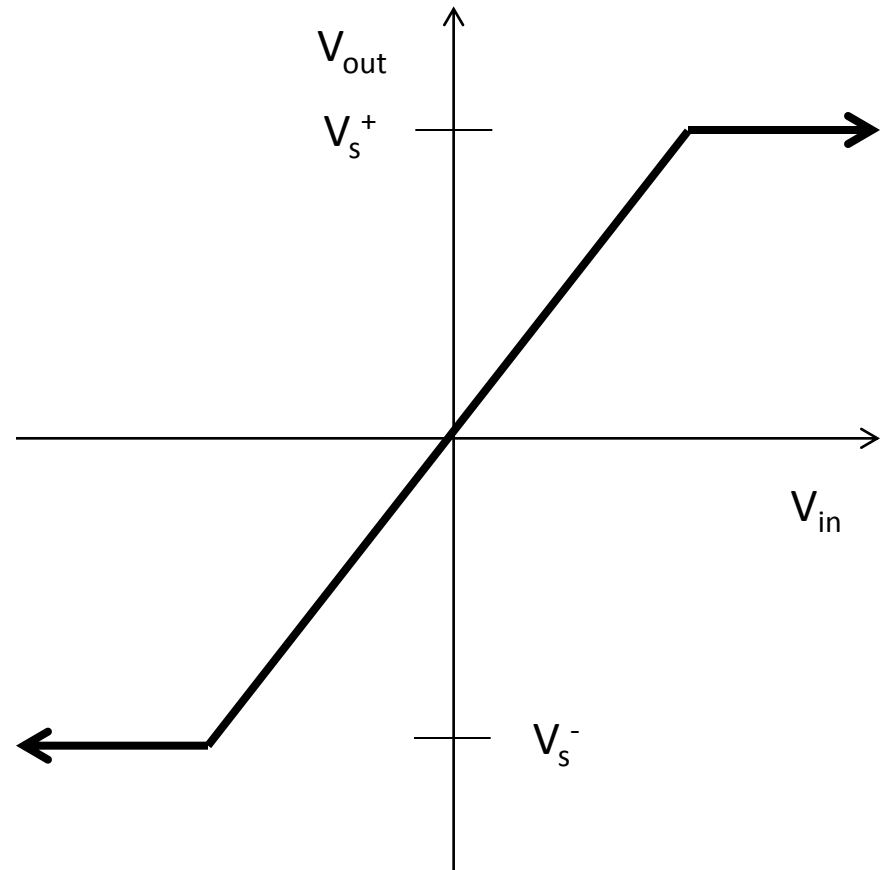
# Op-Amp Saturation

- As mentioned earlier, the maximum output value is the **supply voltage**, positive and negative.
- The gain (G) is the slope between saturation points.




# 741 Op-Amp Schematic

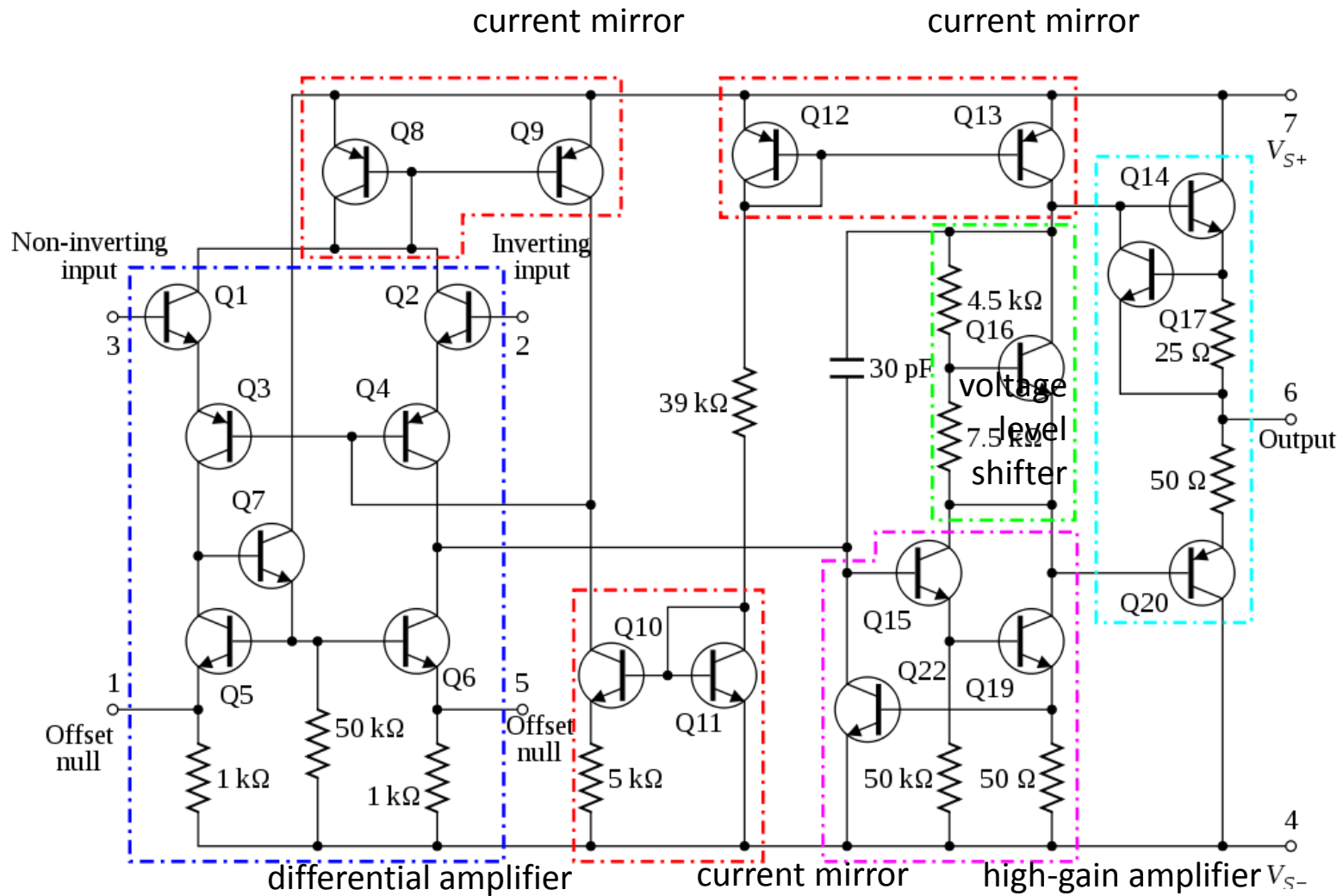


output stage

# Op-Amp Characteristics

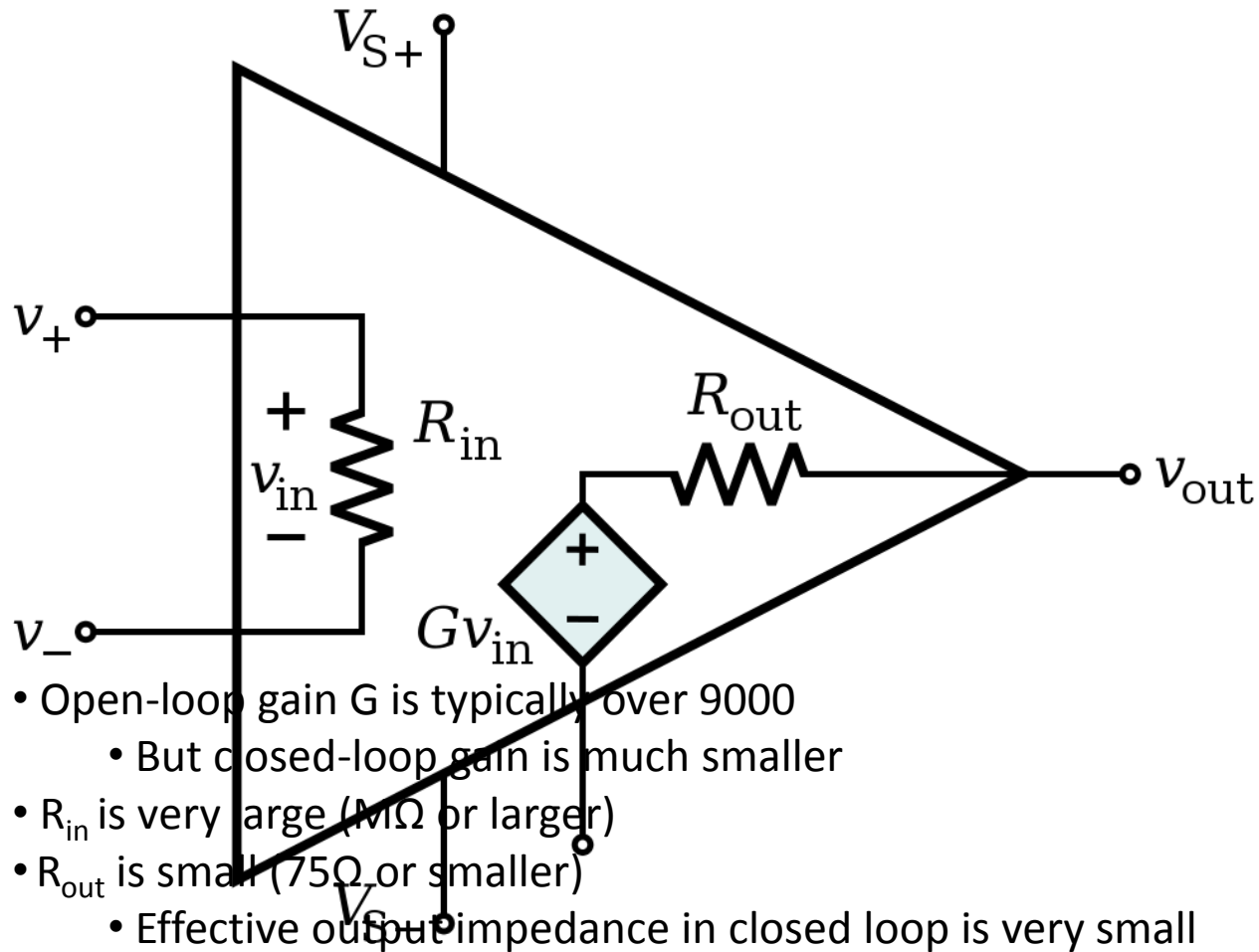


# Ideal Op-Amp Characteristics

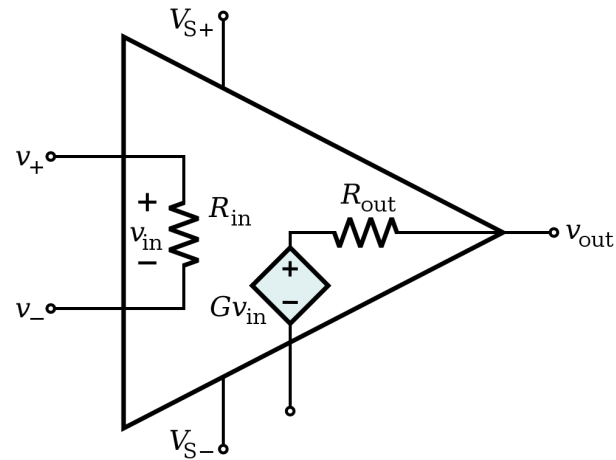

- Open-loop gain  $G$  is infinite
- $R_{in}$  is infinite
  - Zero input current
- $R_{out}$  is zero


# Ideal Op-Amp Analysis

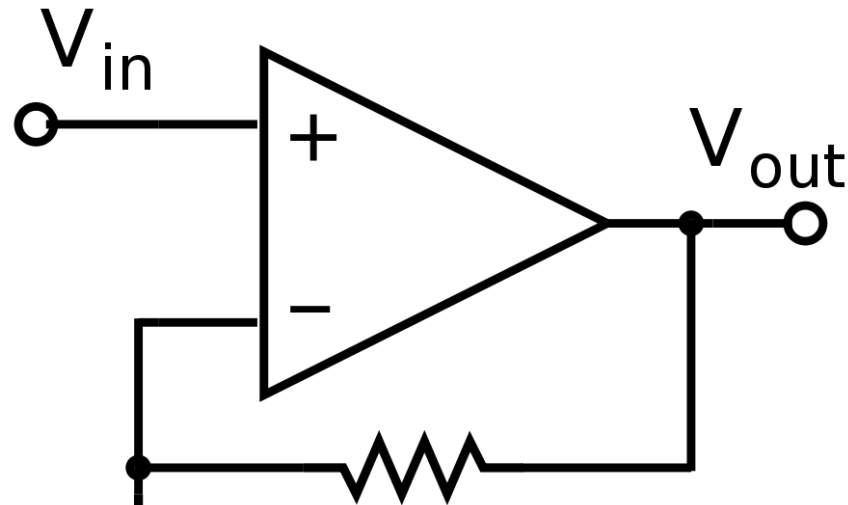


To analyze an op-amp feedback circuit:

- Assume no current flows into either input terminal
- Assume no current flows out of the output terminal
- Constraint:  $V_+ = V_-$

# Inverting Amplifier Analysis

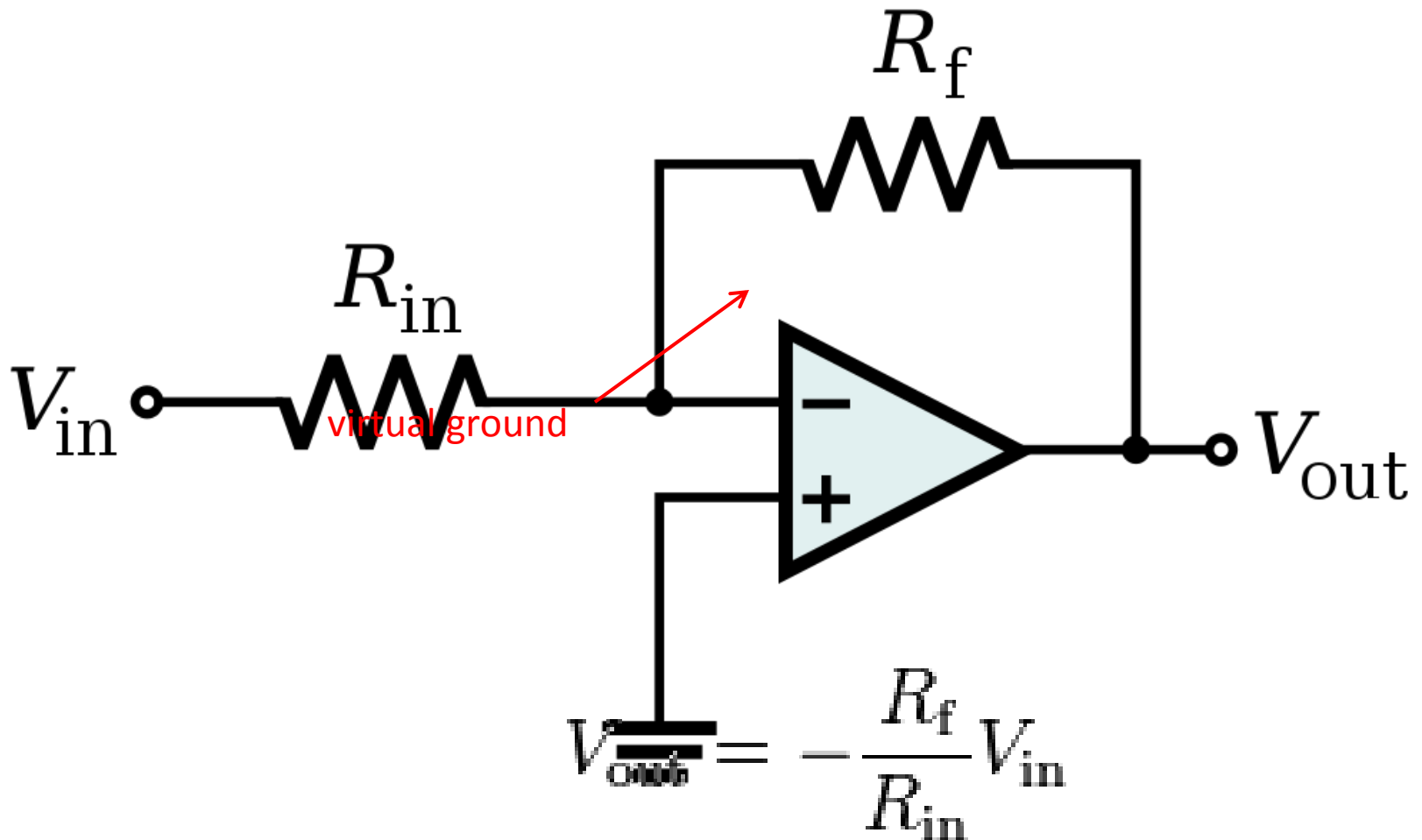


# Non-Inverting Amplifier Analysis

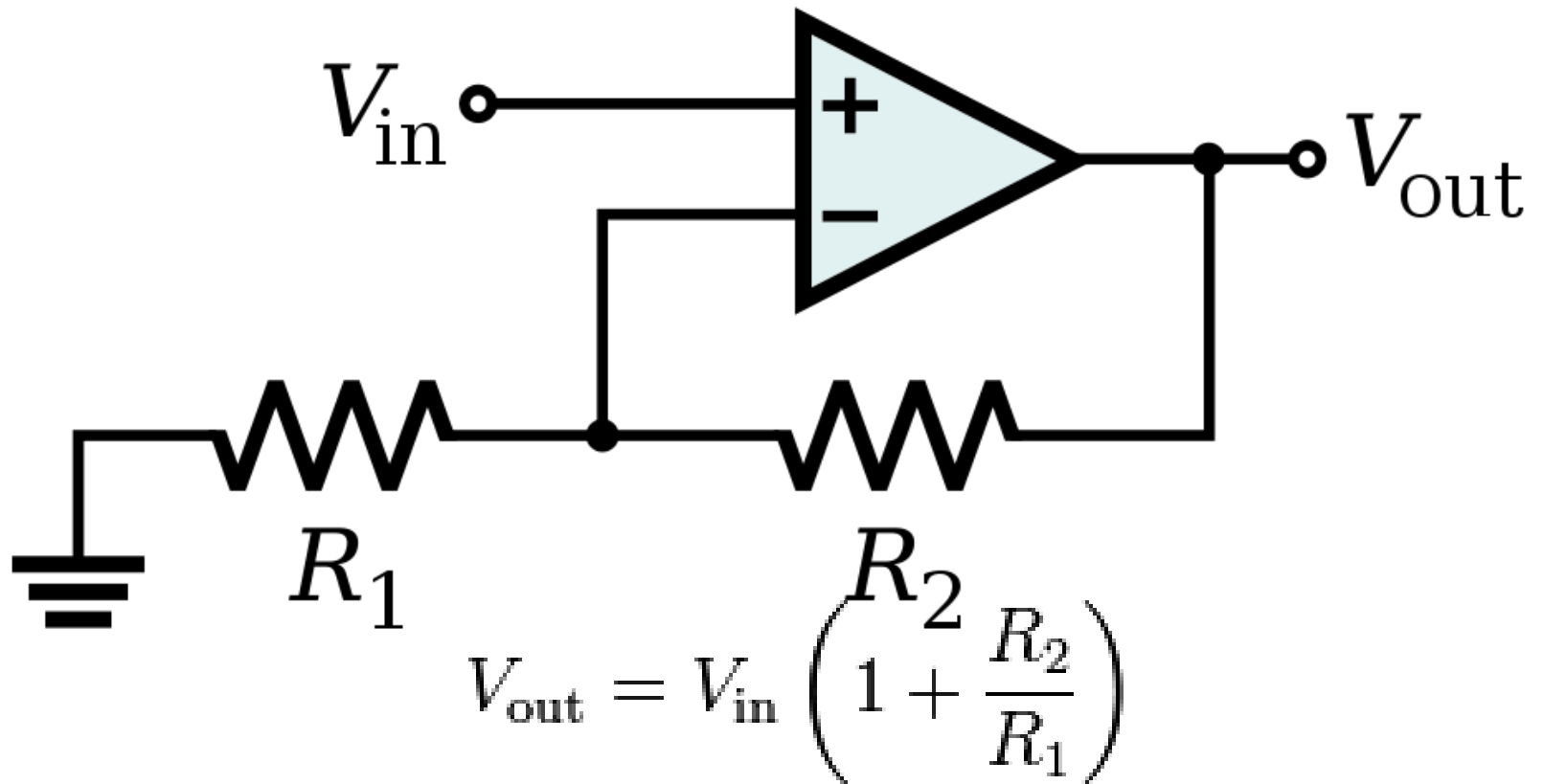





# Op-Amp Buffer

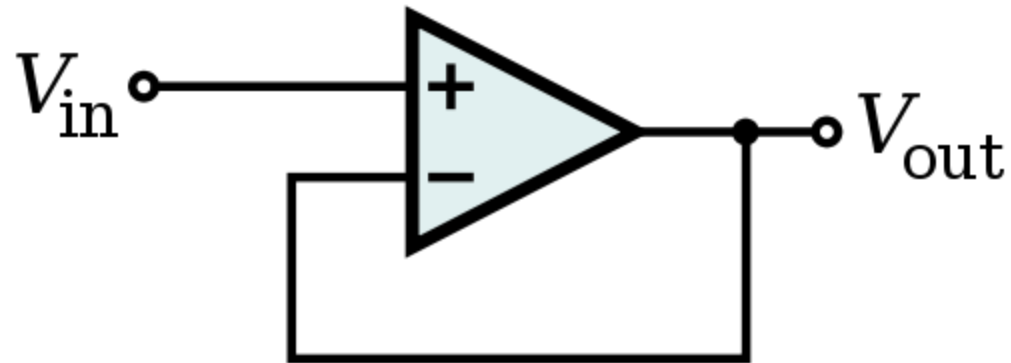

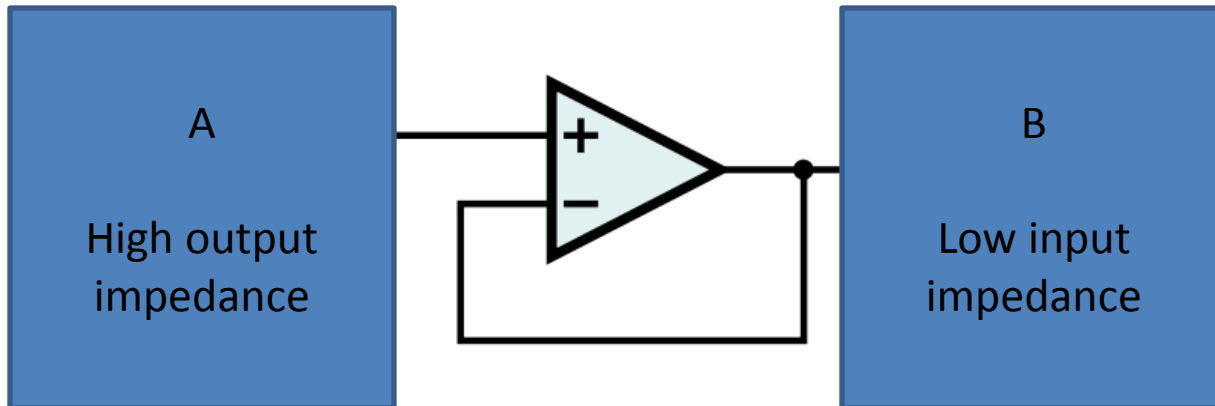
$V_{out} = V_{in}$   
Isolates loading effects



# Op-Amp Differentiator

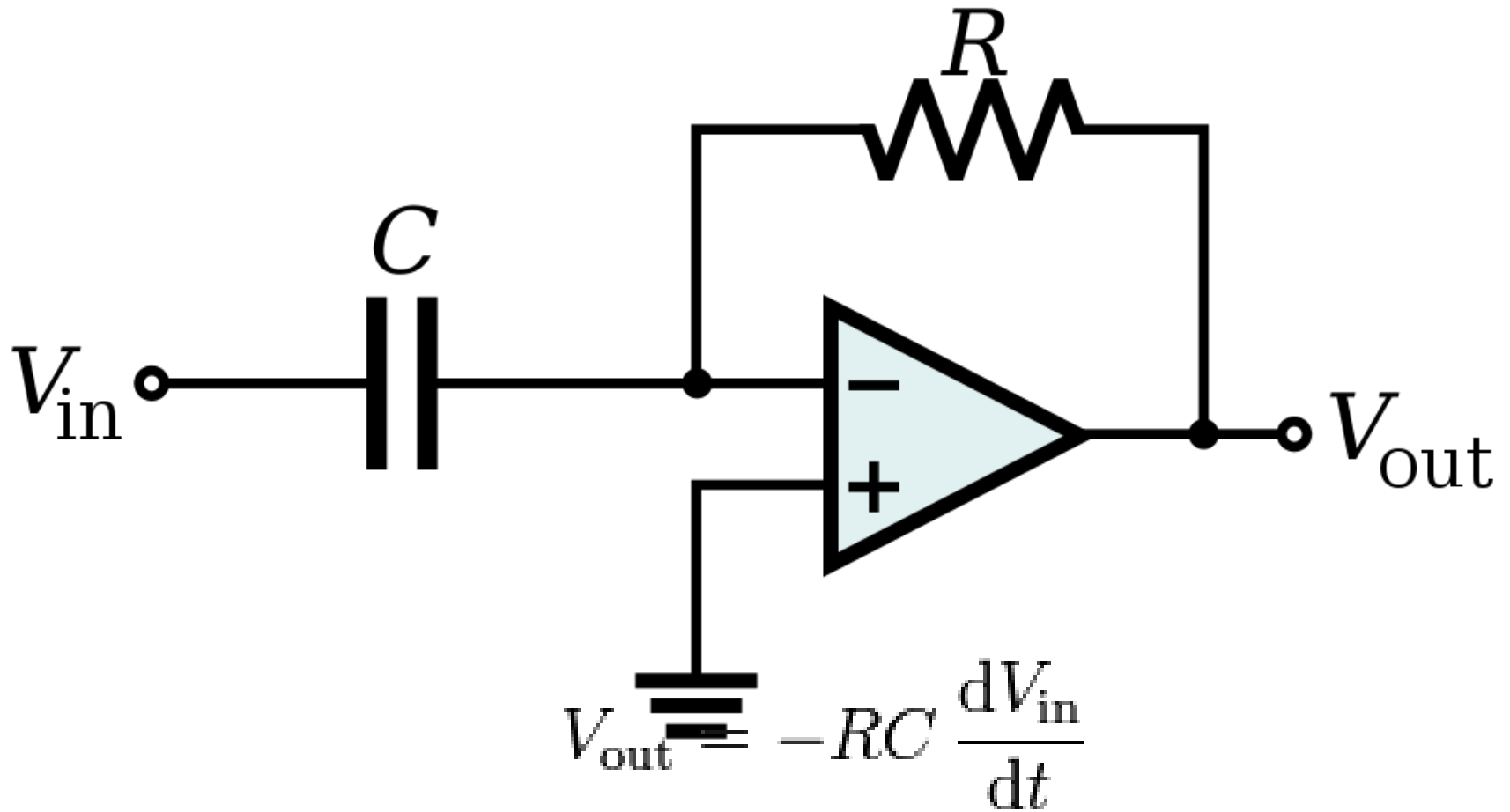


# Op-Amp Integrator

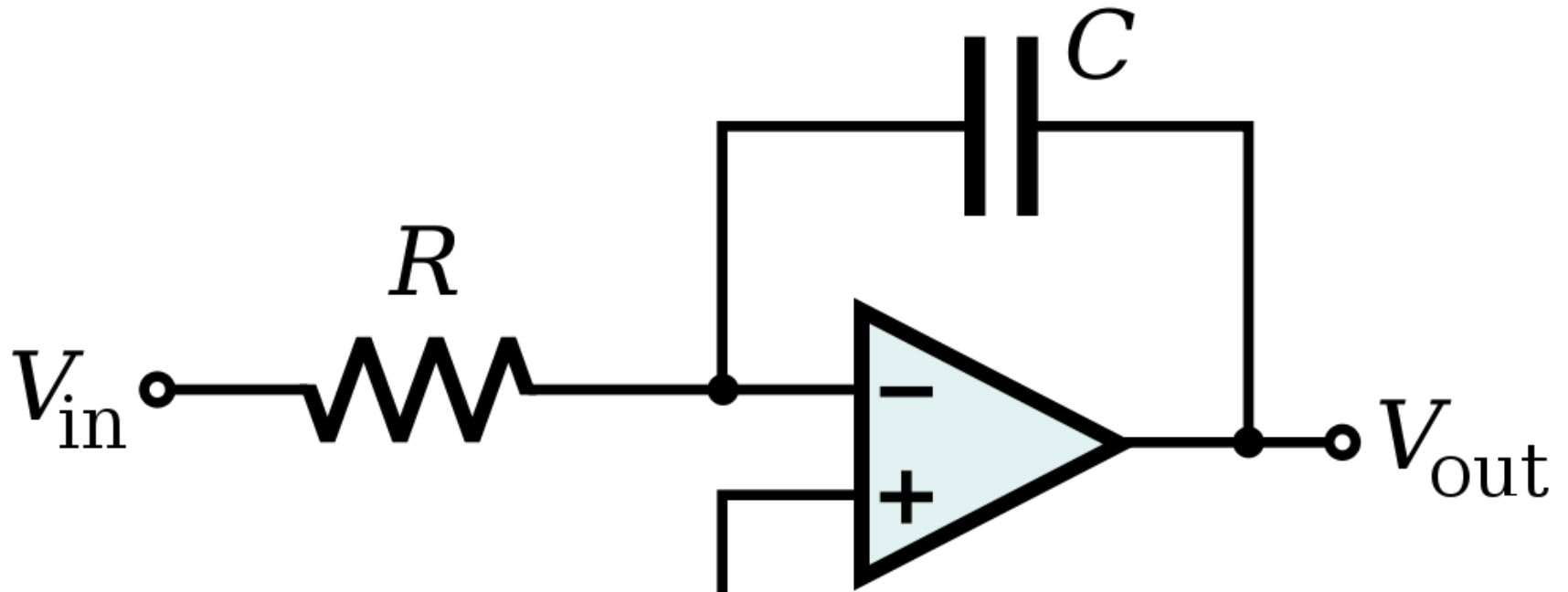


$$V_{out} = - \int_0^t \frac{V_{in}}{RC} dt + V_{initial}$$

# Op-Amp Summing Amplifier

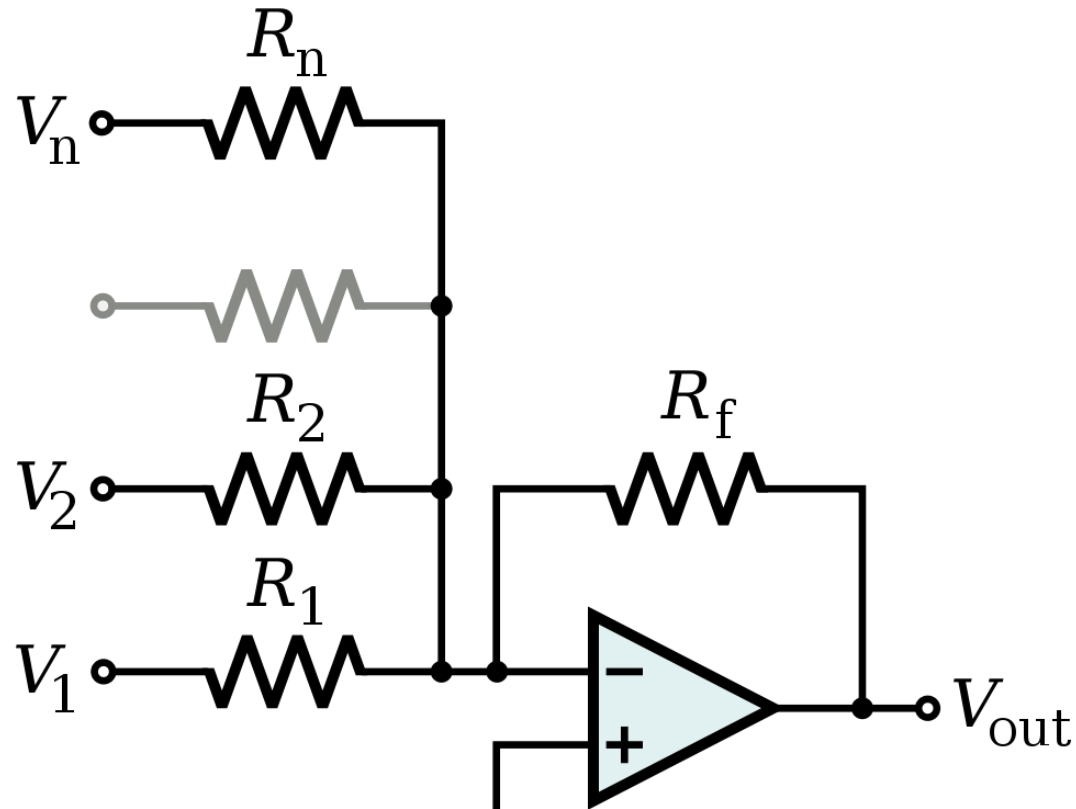

$$V_{out} = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \right)$$

# Op-Amp Differential Amplifier

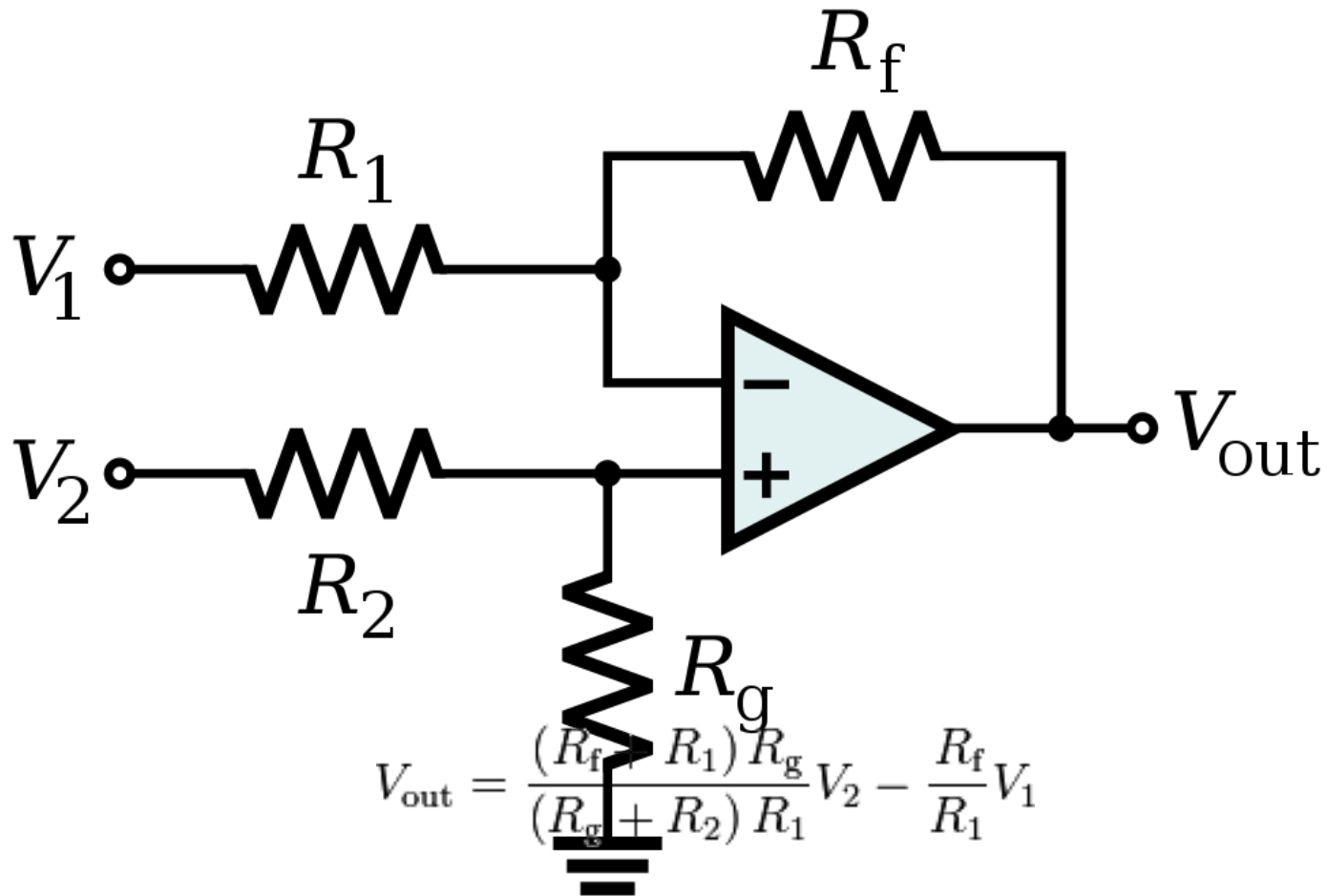

$$V_{out} = \frac{(R_f + R_1) R_g}{(R_g + R_2) R_1} V_2 - \frac{R_f}{R_1} V_1$$

If  $R_1 = R_2$  and  $R_f = R_g$ :

$$V_{out} = \frac{R_f}{R_1} (V_2 - V_1)$$