

BIASING OF BJTS

BJTs

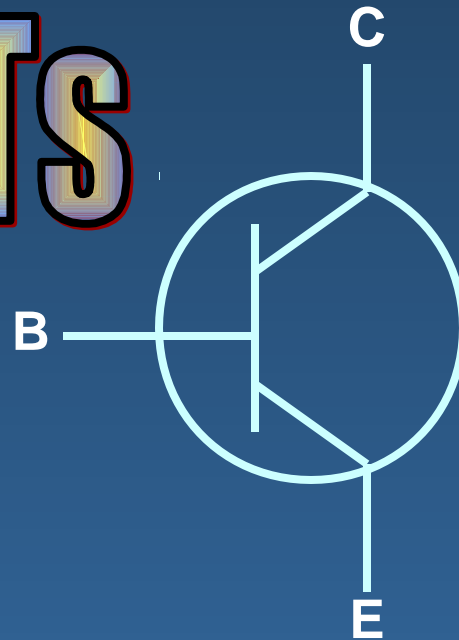



Table of Contents

The Bipolar Junction Transistor	slide 3
BJT Relationships – Equations	slide 4
DC β and DC α	slides 5
BJT Example	slide 6
BJT Transconductance Curve	slide 7
Modes of Operation	slide 8
Three Types of BJT Biasing	slide 9
Common Base	slide 10-11
Common Emitter	slide 12
Common Collector	slide 13
Eber-Moll Model	slides 14-15
Small Signal BJT Equivalent Circuit	slides 16
The Early Effect	slide 17
Early Effect Example	slide 18
Breakdown Voltage	slide 19
Sources	slide 20

The BJT – Bipolar Junction Transistor


β **Note:** It will be very helpful to go through the [Analog Electronics Diodes Tutorial](#) to get information on doping, n-type and p-type materials.

The Two Types of BJT Transistors:

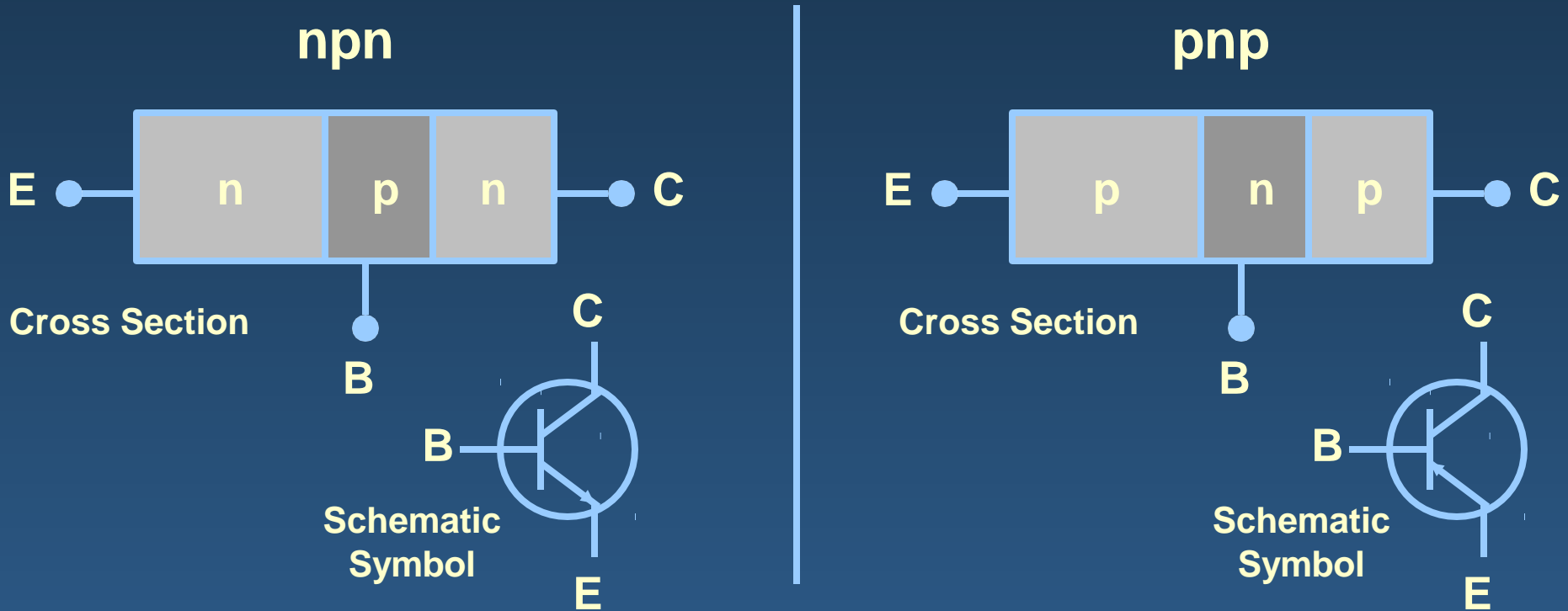

- Collector doping is usually $\sim 10^6$
- Base doping is slightly higher $\sim 10^7 - 10^8$
- Emitter doping is much higher $\sim 10^{15}$


BJT Relationships - Equations

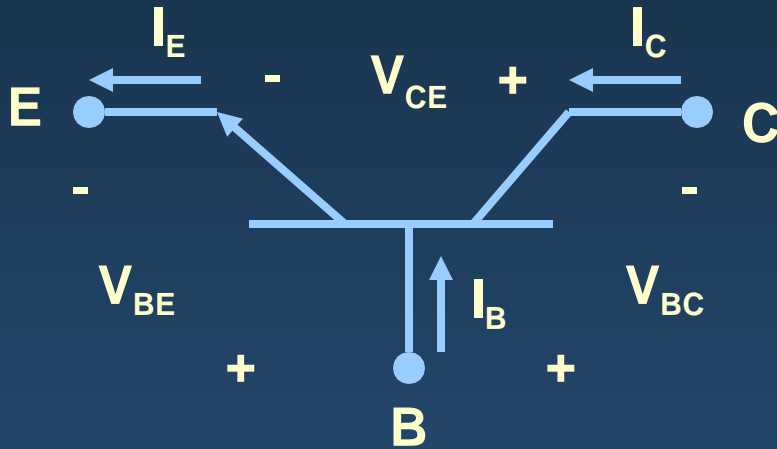

npn

$$I_E = I_B + I_C$$

$$V_{CE} = -V_{BC} + V_{BE}$$

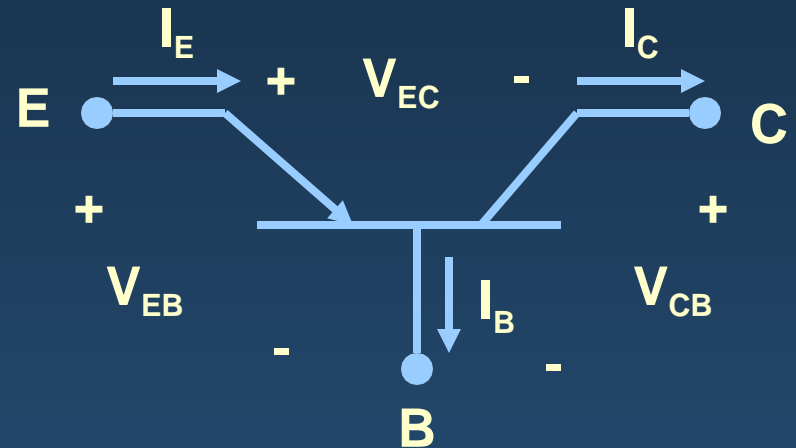

pnp

$$I_E = I_B + I_C$$

$$V_{EC} = V_{EB} - V_{CB}$$

Note: The equations seen above are for the transistor, not the circuit.

DC β and DC α

β = Common-emitter current gain

α = Common-base current gain

$$\beta = \frac{I_C}{I_B} \qquad \alpha = \frac{I_C}{I_E}$$

The relationships between the two parameters are:


$$\alpha = \frac{\beta}{\beta + 1}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

Note: α and β are sometimes referred to as α_{dc} and β_{dc} because the relationships being dealt with in the BJT are DC.

BJT Example

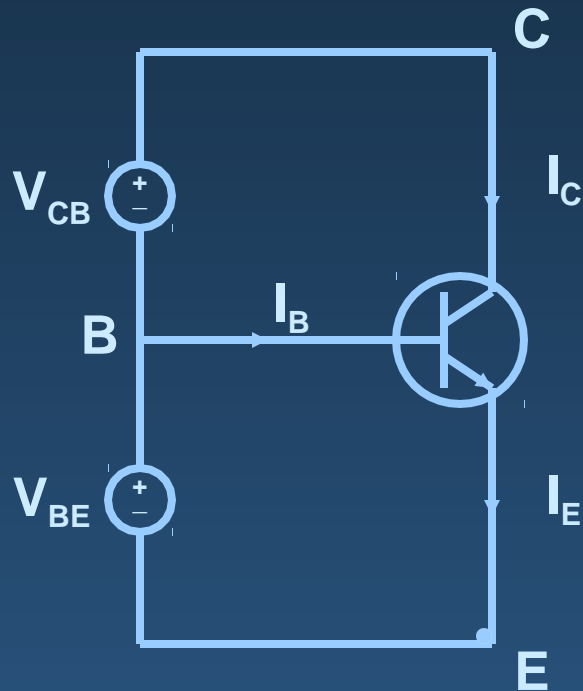Using Common-Base NPN Circuit Configuration



Given: $I_B = 50 \mu\text{A}$, $I_C = 1 \text{ mA}$

Find: I_E , β , and α

Solution:

$$I_E = I_B + I_C = 0.05 \text{ mA} + 1 \text{ mA} = 1.05 \text{ mA}$$

$$\beta = I_C / I_B = 1 \text{ mA} / 0.05 \text{ mA} = 20$$


$$\alpha = I_C / I_E = 1 \text{ mA} / 1.05 \text{ mA} = 0.95238$$

α could also be calculated using the value of β with the formula from the previous slide.

$$\alpha = \frac{\beta}{\beta + 1} = \frac{20}{21} = 0.95238$$

BJT Transconductance Curve

Typical NPN Transistor ¹

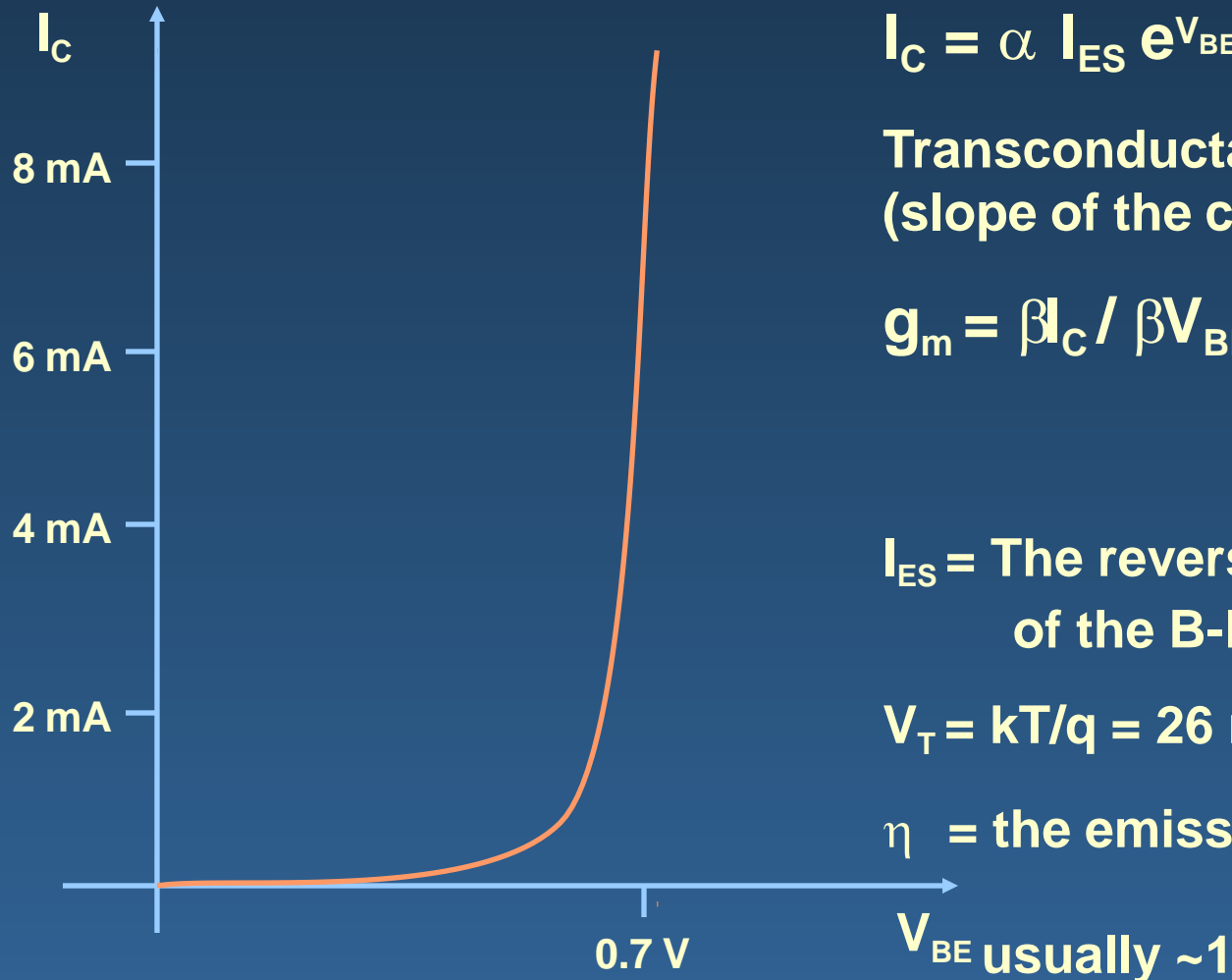

Collector Current:

$$I_C = \alpha I_{ES} e^{V_{BE}/\eta V_T}$$

**Transconductance:
(slope of the curve)**

$$g_m = \beta I_C / \beta V_{BE}$$

I_{ES} = The reverse saturation current
of the B-E Junction.

$$V_T = kT/q = 26 \text{ mV (@ } T=300\text{K)}$$

η = the emission coefficient and is

V_{BE} usually ~ 1

Modes of Operation

Active:

- Most important mode of operation
- Central to amplifier operation
- The region where current curves are practically flat

Saturation:

- Barrier potential of the junctions cancel each other out causing a virtual short

Cutoff:

- Current reduced to zero
- Ideal transistor behaves like an open switch

* Note: There is also a mode of operation called inverse active, but it is rarely used.

Three Types of BJT Biasing

Biasing the transistor refers to applying voltage to get the transistor to achieve certain operating conditions.

Common-Base Biasing (CB) : input = V_{EB} & I_E

output = V_{CB} & I_C

Common-Emitter Biasing (CE): input = V_{BE} & I_B

output = V_{CE} & I_C


Common-Collector Biasing (CC): input = V_{BC} & I_B

output = V_{EC} & I_E

Common-Base


Although the Common-Base configuration is not the most common biasing type, it is often helpful in the understanding of how the BJT works.

Emitter-Current Curves

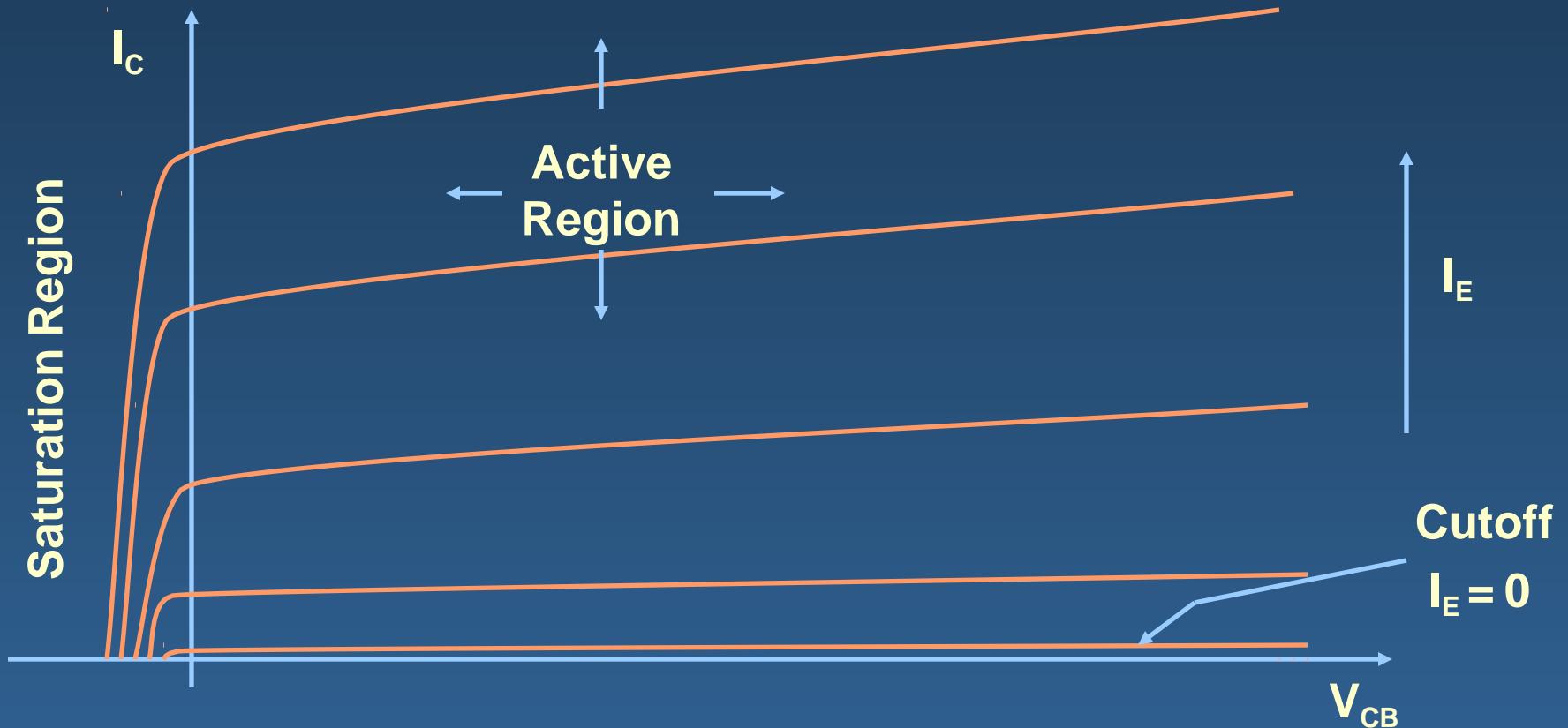

Common-Base

Circuit Diagram: NPN Transistor

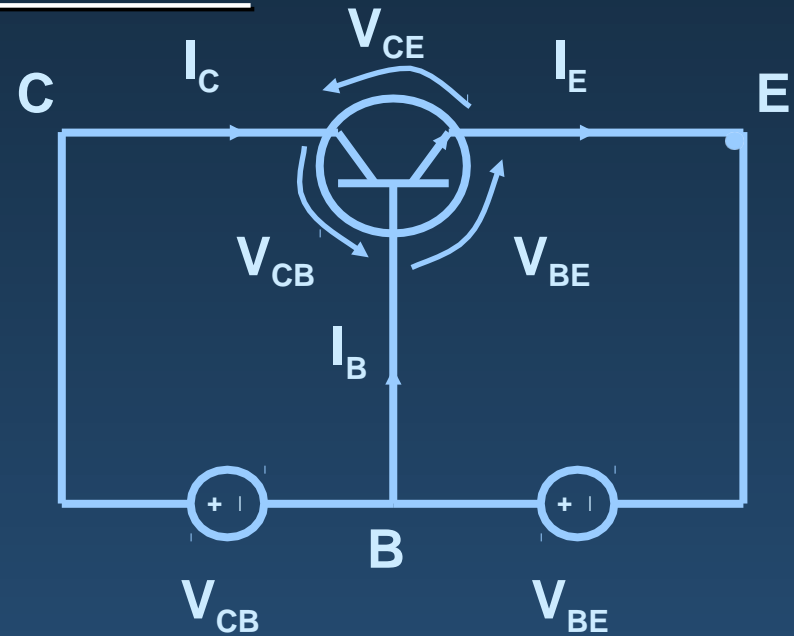


The Table Below lists assumptions that can be made for the attributes of the common-base biased circuit in the different regions of operation. Given for a Silicon NPN transistor.

Region of Operation	I_C	V_{CE}	V_{BE}	V_{CB}	C-B Bias	E-B Bias
Active	βI_B	$=V_{BE}+V_{CE}$	$\sim 0.7V$	$\beta 0V$	Rev.	Fwd.
Saturation	Max	$\sim 0V$	$\sim 0.7V$	$-0.7V < V_{CE} < 0$	Fwd.	Fwd.
Cutoff	~ 0	$=V_{BE}+V_{CE}$	$\beta 0V$	$\beta 0V$	Rev.	None /Rev.

Common-Emitter

Circuit Diagram

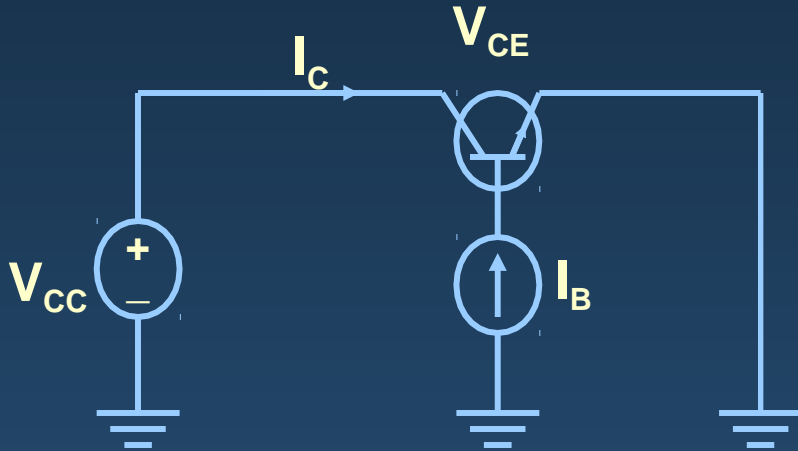

Region of Operation

Description

Active

Small base current controls a large collector current


Saturation

$V_{CE(sat)} \sim 0.2V$, V_{CE} increases with I_C

Cutoff

Achieved by reducing I_B to 0, Ideally, I_C will also equal 0.

Collector-Current Curves

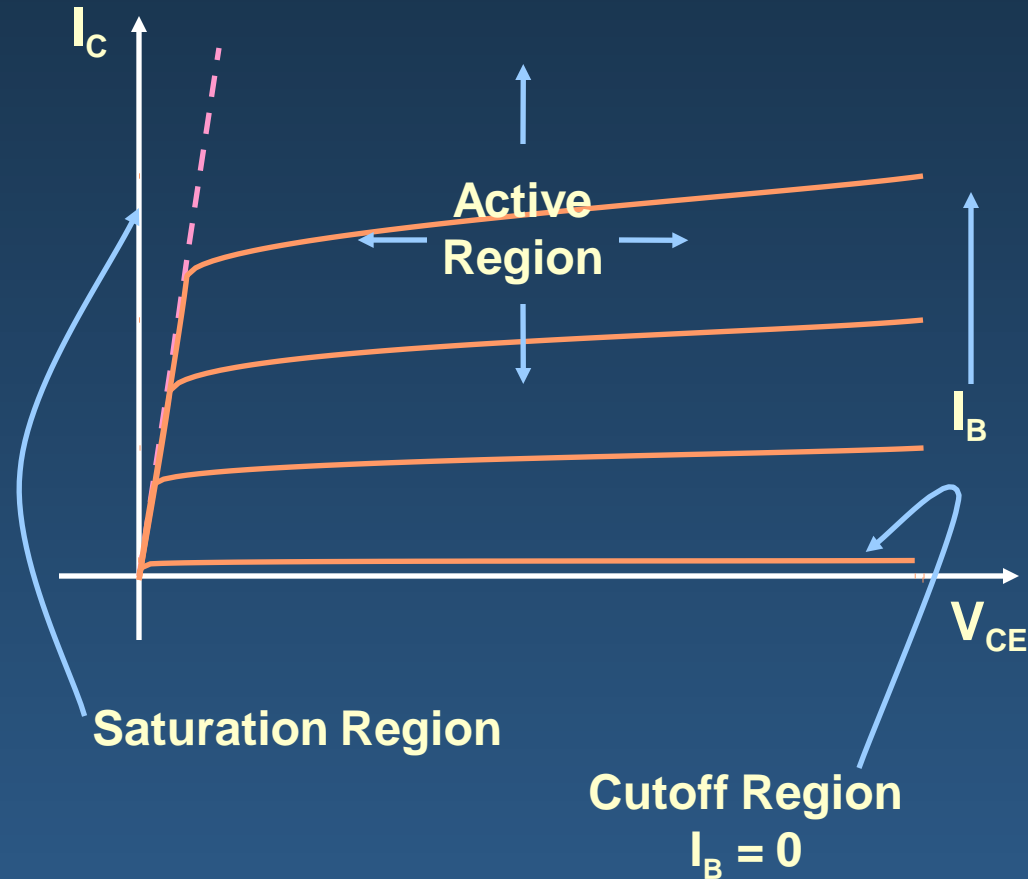


Common-Collector

Emitter-Current Curves


The Common-Collector biasing circuit is basically equivalent to the common-emitter biased circuit except instead of looking at I_C as a function of V_{CE} and I_B we are looking at I_E .

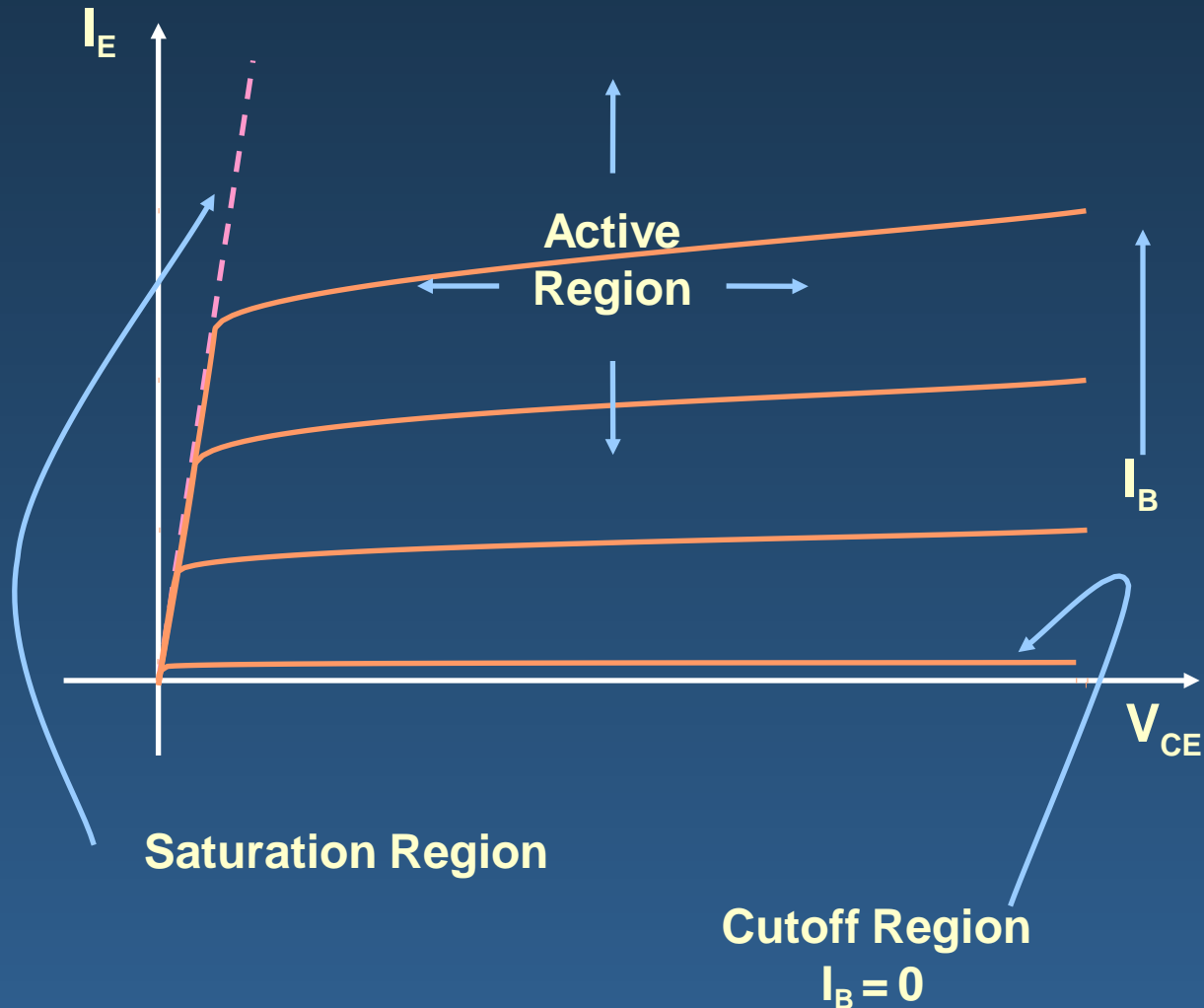Also, since $\alpha \sim 1$, and $\alpha = I_C/I_E$ that means $I_C \sim I_E$



Eber-Moll BJT Model

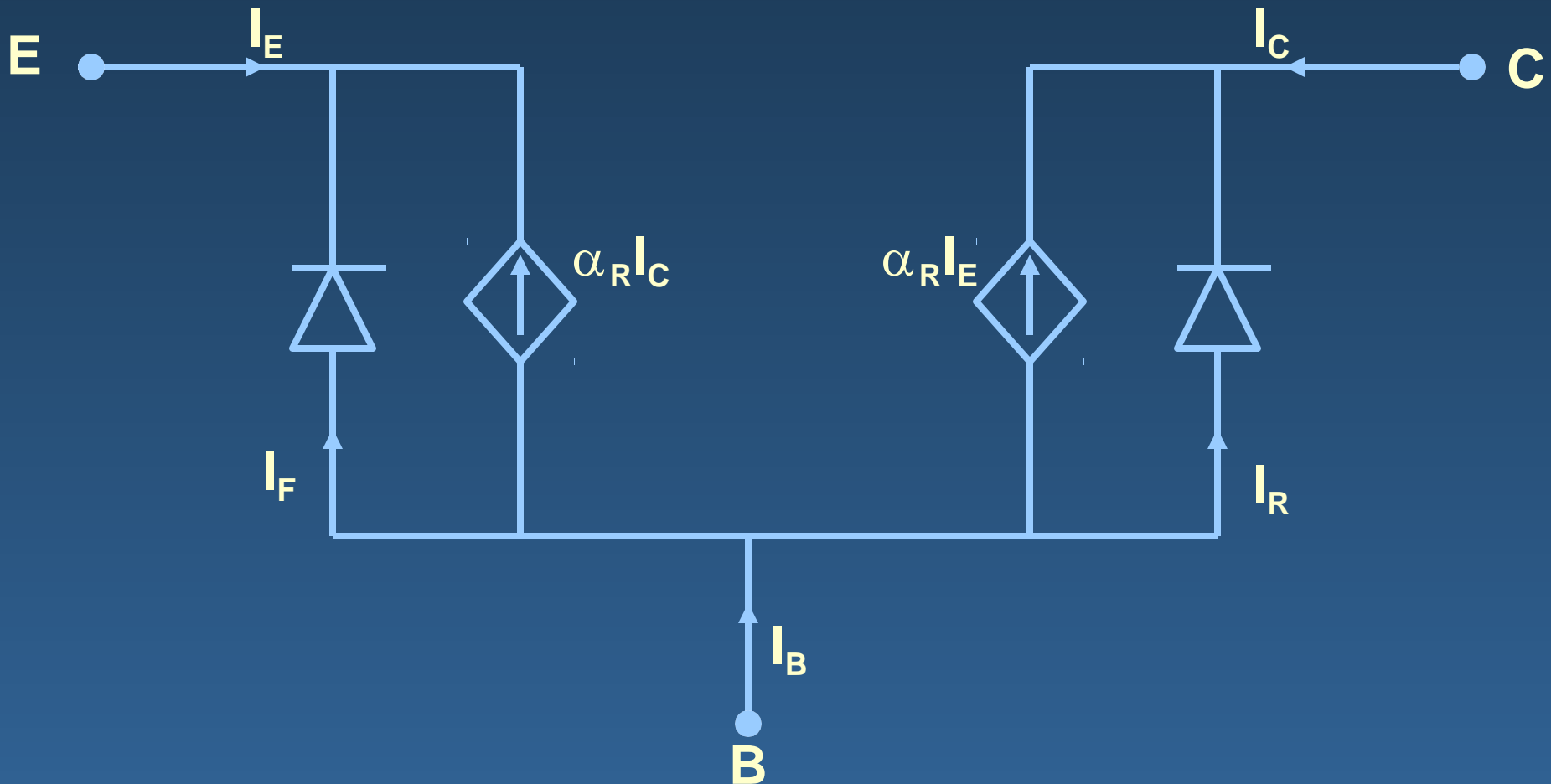The Eber-Moll Model for BJTs is fairly complex, but it is valid in all regions of BJT operation. The circuit diagram below shows all the components of the Eber-Moll Model:



Eber-Moll BJT Model

α_R = Common-base current gain (in forward active mode)

α_F = Common-base current gain (in inverse active mode)

I_{ES} = Reverse-Saturation Current of B-E Junction

I_{CS} = Reverse-Saturation Current of B-C Junction

$$I_C = \alpha_F I_F - I_R \qquad I_B = I_E - I_C$$


$$I_E = I_F - \alpha_R I_R$$

$$I_F = I_{ES} [\exp(qV_{BE}/kT) - 1]$$

$$I_R = I_{CS} [\exp(qV_{BC}/kT) - 1]$$

Small Signal BJT Equivalent Circuit

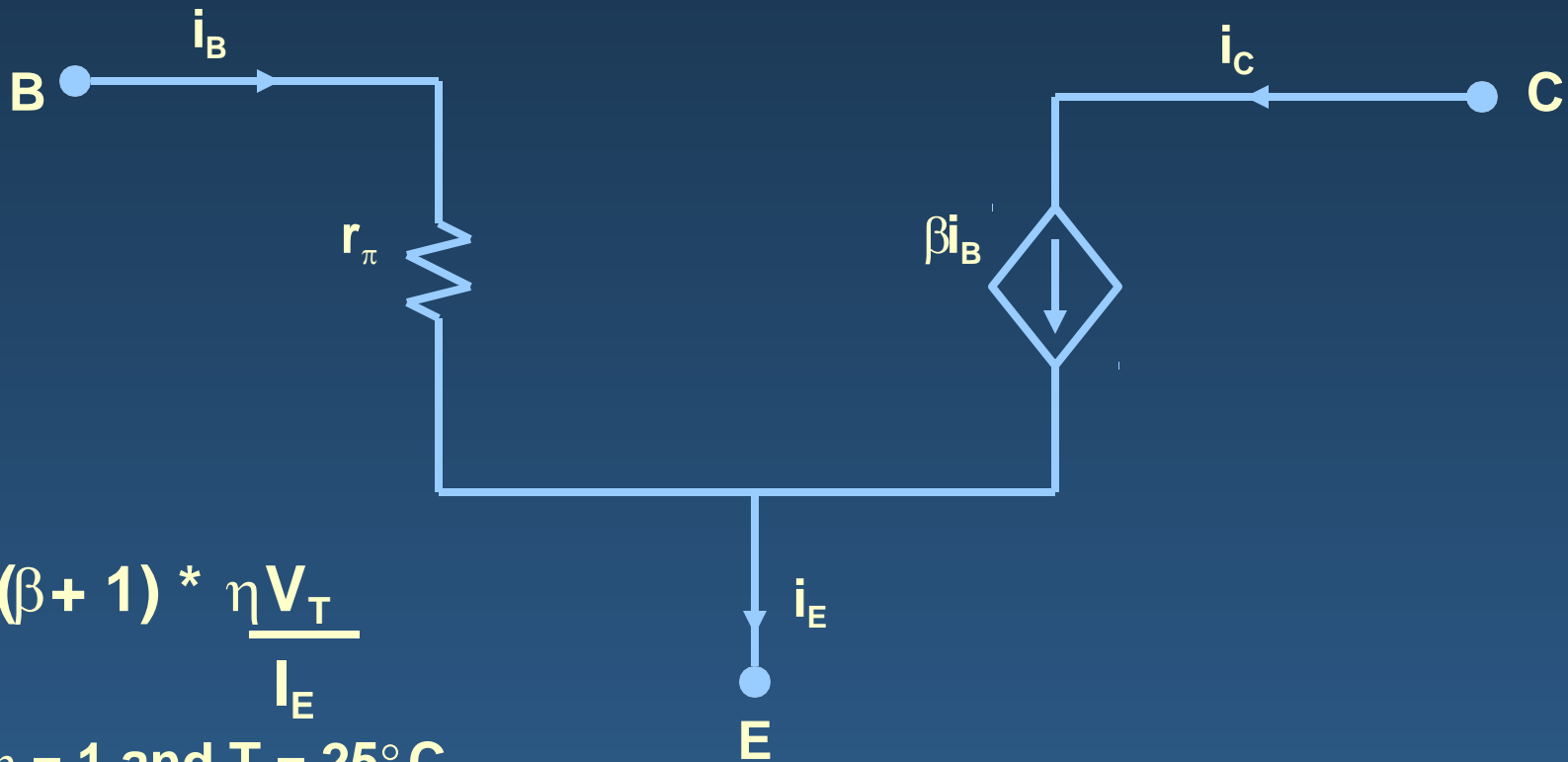The small-signal model can be used when the BJT is in the active region.
The small-signal active-region model for a CB circuit is shown below:



$$r_{\pi} = (\beta + 1) * \frac{\eta V_T}{I_E}$$

@ $\eta = 1$ and $T = 25^{\circ}C$


$$r_{\pi} = (\beta + 1) * \frac{0.026}{I_E}$$

Recall:

$$\beta = I_C / I_B$$

The Early Effect (Early Voltage)

Note: Common-Emitter Configuration

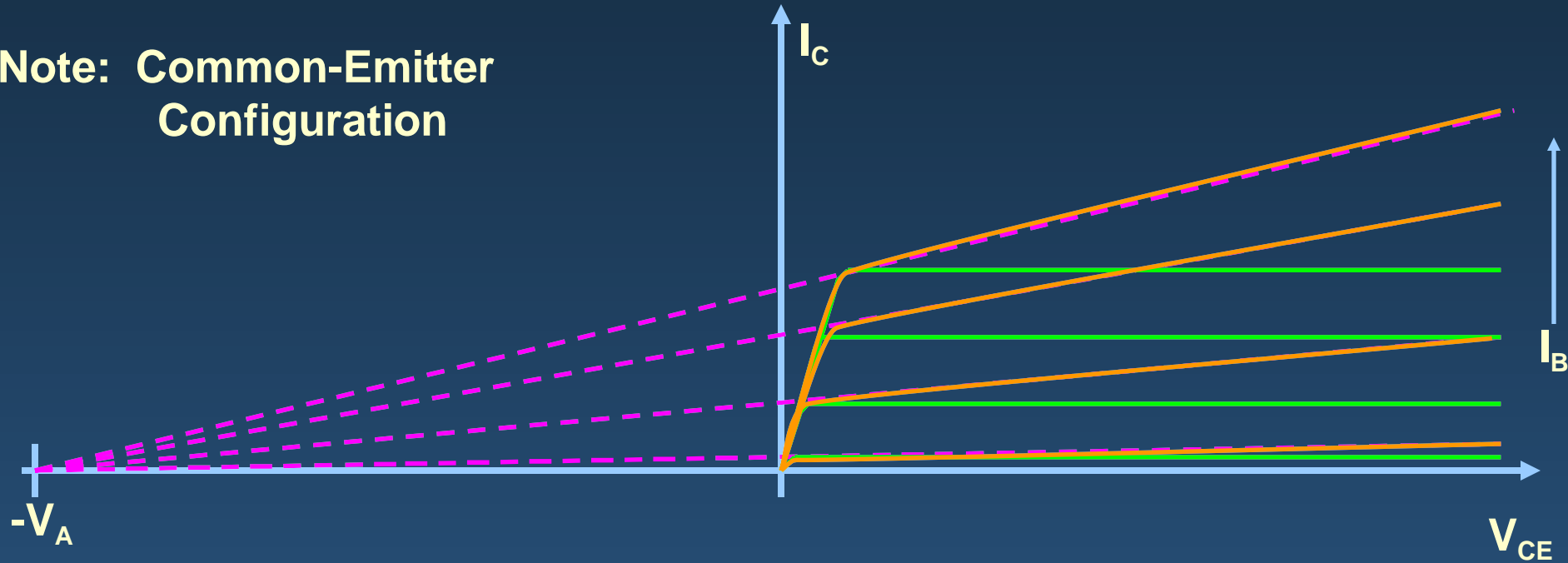

Green = Ideal I_C

Orange = Actual I_C (I_C')


$$I_C' = I_C \left(\frac{V_{CE} + 1}{V_A} \right)$$

Early Effect Example

Given: The common-emitter circuit below with $I_B = 25\mu\text{A}$,
 $V_{CC} = 15\text{V}$, $\beta = 100$ and $V_A = 80$.

Find: a) The ideal collector current
b) The actual collector current

Circuit Diagram

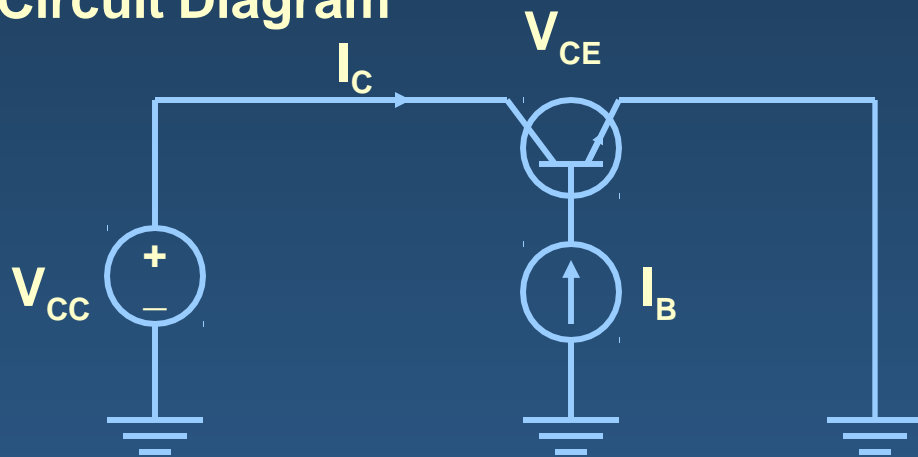

$$\beta = 100 = I_C / I_B$$

a)

$$I_C = 100 * I_B = 100 * (25 \times 10^{-6} \text{ A})$$

$$I_C = 2.5 \text{ mA}$$

$$\text{b) } I_C' = I_C \left(\frac{V_{CE} + 1}{V_A} \right) = 2.5 \times 10^{-3} \left(\frac{15 + 1}{80} \right) = 2.96 \text{ mA}$$

$$I_C' = 2.96 \text{ mA}$$

Breakdown Voltage

The maximum voltage that the BJT can withstand.

BV_{CEO} = The breakdown voltage for a common-emitter biased circuit. This breakdown voltage usually ranges from ~20-1000 Volts.

BV_{CBO} = The breakdown voltage for a common-base biased circuit. This breakdown voltage is usually much higher than BV_{CEO} and has a minimum value of ~60 Volts.

Breakdown Voltage is Determined By:

- The Base Width
- Material Being Used
- Doping Levels
- Biasing Voltage

Sources

Dailey, Denton. Electronic Devices and Circuits, Discrete and Integrated. Prentice Hall, New Jersey: 2001. (pp 84-153)

¹ Figure 3.7, Transconductance curve for a typical npn transistor, pg 90.

Liou, J.J. and Yuan, J.S. Semiconductor Device Physics and Simulation. Plenum Press, New York: 1998.

Neamen, Donald. Semiconductor Physics & Devices. Basic Principles. McGraw-Hill, Boston: 1997. (pp 351-409)

Web Sites

<http://www.infoplease.com/ce6/sci/A0861609.html>